

# 12

## S-Parameters

### 12.1 Scattering Parameters

Linear two-port (and multi-port) networks are characterized by a number of equivalent circuit parameters, such as their transfer matrix, impedance matrix, admittance matrix, and scattering matrix. Fig. 12.1.1 shows a typical two-port network.

 


Fig. 12.1.1 Two-port network.

The *transfer matrix*, also known as the ABCD matrix, relates the voltage and current at port 1 to those at port 2, whereas the *impedance matrix* relates the two voltages  $V_1, V_2$  to the two currents  $I_1, I_2$ †:

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} \quad (\text{transfer matrix}) \quad (12.1.1)$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ -I_2 \end{bmatrix} \quad (\text{impedance matrix})$$

Thus, the transfer and impedance matrices are the  $2 \times 2$  matrices:

$$T = \begin{bmatrix} A & B \\ C & D \end{bmatrix}, \quad Z = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \quad (12.1.2)$$

The *admittance matrix* is simply the inverse of the impedance matrix,  $Y = Z^{-1}$ . The *scattering matrix* relates the *outgoing* waves  $b_1, b_2$  to the *incoming* waves  $a_1, a_2$  that are *incident* on the two-port:

†In the figure,  $I_2$  flows out of port 2, and hence  $-I_2$  flows into it. In the usual convention, both currents  $I_1, I_2$  are taken to flow into their respective ports.

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}, \quad S = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \quad (\text{scattering matrix}) \quad (12.1.3)$$

The matrix elements  $S_{11}, S_{12}, S_{21}, S_{22}$  are referred to as the *scattering parameters* or the *S-parameters*. The parameters  $S_{11}, S_{22}$  have the meaning of reflection coefficients, and  $S_{21}, S_{12}$ , the meaning of transmission coefficients.

The many properties and uses of the S-parameters in applications are discussed in [571–610]. One particularly nice overview is the HP application note AN-95-1 by Anderson [586] and is available on the web [853].

We have already seen several examples of transfer, impedance, and scattering matrices. Eq. (9.7.6) or (9.7.7) is an example of a transfer matrix and (9.8.1) is the corresponding impedance matrix. The transfer and scattering matrices of multilayer structures, Eqs. (5.6.23) and (5.6.37), are more complicated examples.

The traveling wave variables  $a_1, b_1$  at port 1 and  $a_2, b_2$  at port 2 are defined in terms of  $V_1, I_1$  and  $V_2, I_2$  and a real-valued positive reference impedance  $Z_0$  as follows:

$$\begin{aligned} a_1 &= \frac{V_1 + Z_0 I_1}{2\sqrt{Z_0}} & a_2 &= \frac{V_2 - Z_0 I_2}{2\sqrt{Z_0}} \\ b_1 &= \frac{V_1 - Z_0 I_1}{2\sqrt{Z_0}} & b_2 &= \frac{V_2 + Z_0 I_2}{2\sqrt{Z_0}} \end{aligned} \quad (\text{traveling waves}) \quad (12.1.4)$$

The definitions at port 2 appear different from those at port 1, but they are really the same if expressed in terms of the incoming current  $-I_2$ :

$$\begin{aligned} a_2 &= \frac{V_2 - Z_0 I_2}{2\sqrt{Z_0}} = \frac{V_2 + Z_0 (-I_2)}{2\sqrt{Z_0}} \\ b_2 &= \frac{V_2 + Z_0 I_2}{2\sqrt{Z_0}} = \frac{V_2 - Z_0 (-I_2)}{2\sqrt{Z_0}} \end{aligned}$$

The term *traveling waves* is justified below. Eqs. (12.1.4) may be inverted to express the voltages and currents in terms of the wave variables:

$$\begin{aligned} V_1 &= \sqrt{Z_0} (a_1 + b_1) & V_2 &= \sqrt{Z_0} (a_2 + b_2) \\ I_1 &= \frac{1}{\sqrt{Z_0}} (a_1 - b_1) & I_2 &= \frac{1}{\sqrt{Z_0}} (b_2 - a_2) \end{aligned} \quad (12.1.5)$$

In practice, the reference impedance is chosen to be  $Z_0 = 50$  ohm. At lower frequencies the transfer and impedance matrices are commonly used, but at microwave frequencies they become difficult to measure and therefore, the scattering matrix description is preferred.

The S-parameters can be measured by embedding the two-port network (the device-under-test, or, DUT) in a transmission line whose ends are connected to a network analyzer. Fig. 12.1.2 shows the experimental setup.

A typical network analyzer can measure S-parameters over a large frequency range, for example, the HP 8720D vector network analyzer covers the range from 50 MHz to

40 GHz. Frequency resolution is typically 1 Hz and the results can be displayed either on a Smith chart or as a conventional gain versus frequency graph.

 


Fig. 12.1.2 Device under test connected to network analyzer.

Fig. 12.1.3 shows more details of the connection. The generator and load impedances are configured by the network analyzer. The connections can be reversed, with the generator connected to port 2 and the load to port 1.

 


Fig. 12.1.3 Two-port network under test.

The two line segments of lengths  $l_1, l_2$  are assumed to have characteristic impedance equal to the reference impedance  $Z_0$ . Then, the wave variables  $a_1, b_1$  and  $a_2, b_2$  are recognized as normalized versions of forward and backward *traveling waves*. Indeed, according to Eq. (9.7.8), we have:

$$\begin{aligned}
 a_1 &= \frac{V_1 + Z_0 I_1}{2\sqrt{Z_0}} = \frac{1}{\sqrt{Z_0}} V_{1+} & a_2 &= \frac{V_2 - Z_0 I_2}{2\sqrt{Z_0}} = \frac{1}{\sqrt{Z_0}} V_{2-} \\
 b_1 &= \frac{V_1 - Z_0 I_1}{2\sqrt{Z_0}} = \frac{1}{\sqrt{Z_0}} V_{1-} & b_2 &= \frac{V_2 + Z_0 I_2}{2\sqrt{Z_0}} = \frac{1}{\sqrt{Z_0}} V_{2+}
 \end{aligned}
 \tag{12.1.6}$$

Thus,  $a_1$  is essentially the incident wave at port 1 and  $b_1$  the corresponding reflected wave. Similarly,  $a_2$  is incident from the right onto port 2 and  $b_2$  is the reflected wave from port 2.

The network analyzer measures the waves  $a'_1, b'_1$  and  $a'_2, b'_2$  at the generator and load ends of the line segments, as shown in Fig. 12.1.3. From these, the waves at the inputs of the two-port can be determined. Assuming lossless segments and using the propagation matrices (9.7.7), we have:

$$\begin{bmatrix} a_1 \\ b_1 \end{bmatrix} = \begin{bmatrix} e^{-j\delta_1} & 0 \\ 0 & e^{j\delta_1} \end{bmatrix} \begin{bmatrix} a'_1 \\ b'_1 \end{bmatrix}, \quad \begin{bmatrix} a_2 \\ b_2 \end{bmatrix} = \begin{bmatrix} e^{-j\delta_2} & 0 \\ 0 & e^{j\delta_2} \end{bmatrix} \begin{bmatrix} a'_2 \\ b'_2 \end{bmatrix}
 \tag{12.1.7}$$

where  $\delta_1 = \beta l_1$  and  $\delta_2 = \beta l_2$  are the phase lengths of the segments. Eqs. (12.1.7) can be rearranged into the forms:

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = D \begin{bmatrix} b'_1 \\ b'_2 \end{bmatrix}, \quad \begin{bmatrix} a'_1 \\ a'_2 \end{bmatrix} = D \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}, \quad D = \begin{bmatrix} e^{j\delta_1} & 0 \\ 0 & e^{j\delta_2} \end{bmatrix}$$

The network analyzer measures the corresponding  $S$ -parameters of the primed variables, that is,

$$\begin{bmatrix} b'_1 \\ b'_2 \end{bmatrix} = \begin{bmatrix} S'_{11} & S'_{12} \\ S'_{21} & S'_{22} \end{bmatrix} \begin{bmatrix} a'_1 \\ a'_2 \end{bmatrix}, \quad S' = \begin{bmatrix} S'_{11} & S'_{12} \\ S'_{21} & S'_{22} \end{bmatrix} \quad (\text{measured } S\text{-matrix}) \tag{12.1.8}$$

The  $S$ -matrix of the two-port can be obtained then from:

$$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = D \begin{bmatrix} b'_1 \\ b'_2 \end{bmatrix} = DS' \begin{bmatrix} a'_1 \\ a'_2 \end{bmatrix} = DS'D \begin{bmatrix} a_1 \\ a_2 \end{bmatrix} \Rightarrow S = DS'D$$

or, more explicitly,

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \begin{bmatrix} e^{j\delta_1} & 0 \\ 0 & e^{j\delta_2} \end{bmatrix} \begin{bmatrix} S'_{11} & S'_{12} \\ S'_{21} & S'_{22} \end{bmatrix} \begin{bmatrix} e^{j\delta_1} & 0 \\ 0 & e^{j\delta_2} \end{bmatrix} \\
 = \begin{bmatrix} S'_{11}e^{2j\delta_1} & S'_{12}e^{j(\delta_1+\delta_2)} \\ S'_{21}e^{j(\delta_1+\delta_2)} & S'_{22}e^{2j\delta_2} \end{bmatrix}
 \tag{12.1.9}$$

Thus, changing the points along the transmission lines at which the  $S$ -parameters are measured introduces only phase changes in the parameters.

Without loss of generality, we may replace the extended circuit of Fig. 12.1.3 with the one shown in Fig. 12.1.4 with the understanding that either we are using the extended two-port parameters  $S'$ , or, equivalently, the generator and segment  $l_1$  have been replaced by their Thévenin equivalents, and the load impedance has been replaced by its propagated version to distance  $l_2$ .

 


Fig. 12.1.4 Two-port network connected to generator and load.

The actual measurements of the  $S$ -parameters are made by connecting to a matched load,  $Z_L = Z_0$ . Then, there will be no reflected waves from the load,  $a_2 = 0$ , and the  $S$ -matrix equations will give:

$$\begin{aligned} b_1 = S_{11}a_1 + S_{12}a_2 = S_{11}a_1 &\Rightarrow S_{11} = \left. \frac{b_1}{a_1} \right|_{Z_L=Z_0} = \text{reflection coefficient} \\ b_2 = S_{21}a_1 + S_{22}a_2 = S_{21}a_1 &\Rightarrow S_{21} = \left. \frac{b_2}{a_1} \right|_{Z_L=Z_0} = \text{transmission coefficient} \end{aligned}$$

Reversing the roles of the generator and load, one can measure in the same way the parameters  $S_{12}$  and  $S_{22}$ .

## 12.2 Power Flow

Power flow into and out of the two-port is expressed very simply in terms of the traveling wave amplitudes. Using the inverse relationships (12.1.5), we find:

$$\begin{aligned} \frac{1}{2} \operatorname{Re}[V_1^* I_1] &= \frac{1}{2} |a_1|^2 - \frac{1}{2} |b_1|^2 \\ -\frac{1}{2} \operatorname{Re}[V_2^* I_2] &= \frac{1}{2} |a_2|^2 - \frac{1}{2} |b_2|^2 \end{aligned} \quad (12.2.1)$$

The left-hand sides represent the power flow *into* ports 1 and 2. The right-hand sides represent the difference between the power incident on a port and the power reflected from it. The quantity  $\operatorname{Re}[V_2^* I_2]/2$  represents the power transferred to the load.

Another way of phrasing these is to say that part of the incident power on a port gets reflected and part enters the port:

$$\begin{aligned} \frac{1}{2} |a_1|^2 &= \frac{1}{2} |b_1|^2 + \frac{1}{2} \operatorname{Re}[V_1^* I_1] \\ \frac{1}{2} |a_2|^2 &= \frac{1}{2} |b_2|^2 + \frac{1}{2} \operatorname{Re}[V_2^* (-I_2)] \end{aligned} \quad (12.2.2)$$

One of the reasons for normalizing the traveling wave amplitudes by  $\sqrt{Z_0}$  in the definitions (12.1.4) was precisely this simple way of expressing the incident and reflected powers from a port.

If the two-port is lossy, the power lost in it will be the difference between the power entering port 1 and the power leaving port 2, that is,

$$P_{\text{loss}} = \frac{1}{2} \operatorname{Re}[V_1^* I_1] - \frac{1}{2} \operatorname{Re}[V_2^* I_2] = \frac{1}{2} |a_1|^2 + \frac{1}{2} |a_2|^2 - \frac{1}{2} |b_1|^2 - \frac{1}{2} |b_2|^2$$

Noting that  $\mathbf{a}^\dagger \mathbf{a} = |a_1|^2 + |a_2|^2$  and  $\mathbf{b}^\dagger \mathbf{b} = |b_1|^2 + |b_2|^2$ , and writing  $\mathbf{b}^\dagger \mathbf{b} = \mathbf{a}^\dagger \mathbf{S}^\dagger \mathbf{S} \mathbf{a}$ , we may express this relationship in terms of the scattering matrix:

$$P_{\text{loss}} = \frac{1}{2} \mathbf{a}^\dagger \mathbf{a} - \frac{1}{2} \mathbf{b}^\dagger \mathbf{b} = \frac{1}{2} \mathbf{a}^\dagger \mathbf{a} - \frac{1}{2} \mathbf{a}^\dagger \mathbf{S}^\dagger \mathbf{S} \mathbf{a} = \frac{1}{2} \mathbf{a}^\dagger (\mathbf{I} - \mathbf{S}^\dagger \mathbf{S}) \mathbf{a} \quad (12.2.3)$$

For a lossy two-port, the power loss is positive, which implies that the matrix  $\mathbf{I} - \mathbf{S}^\dagger \mathbf{S}$  must be positive definite. If the two-port is lossless,  $P_{\text{loss}} = 0$ , the  $S$ -matrix will be *unitary*, that is,  $\mathbf{S}^\dagger \mathbf{S} = \mathbf{I}$ .

We already saw examples of such unitary scattering matrices in the cases of the equal travel-time multilayer dielectric structures and their equivalent quarter wavelength multisection transformers.

## 12.3 Parameter Conversions

It is straightforward to derive the relationships that allow one to pass from one parameter set to another. For example, starting with the transfer matrix, we have:

$$\begin{aligned} V_1 = AV_2 + BI_2 &\Rightarrow V_1 = A\left(\frac{1}{C}I_1 - \frac{D}{C}I_2\right) + BI_2 = \frac{A}{C}I_1 - \frac{AD - BC}{C}I_2 \\ I_1 = CV_2 + DI_2 &\Rightarrow V_2 = \frac{1}{C}I_1 - \frac{D}{C}I_2 \end{aligned}$$

The coefficients of  $I_1, I_2$  are the impedance matrix elements. The steps are reversible, and we summarize the final relationships below:

$$\begin{aligned} Z &= \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \frac{1}{C} \begin{bmatrix} A & AD - BC \\ 1 & D \end{bmatrix} \\ T &= \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \frac{1}{Z_{21}} \begin{bmatrix} Z_{11} & Z_{11}Z_{22} - Z_{12}Z_{21} \\ 1 & Z_{22} \end{bmatrix} \end{aligned} \quad (12.3.1)$$

We note the determinants  $\det(T) = AD - BC$  and  $\det(Z) = Z_{11}Z_{22} - Z_{12}Z_{21}$ . The relationship between the scattering and impedance matrices is also straightforward to derive. We define the  $2 \times 1$  vectors:

$$\mathbf{V} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}, \quad \mathbf{I} = \begin{bmatrix} I_1 \\ -I_2 \end{bmatrix}, \quad \mathbf{a} = \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}, \quad \mathbf{b} = \begin{bmatrix} b_1 \\ b_2 \end{bmatrix} \quad (12.3.2)$$

Then, the definitions (12.1.4) can be written compactly as:

$$\begin{aligned} \mathbf{a} &= \frac{1}{2\sqrt{Z_0}} (\mathbf{V} + Z_0 \mathbf{I}) = \frac{1}{2\sqrt{Z_0}} (\mathbf{Z} + Z_0 \mathbf{I}) \mathbf{I} \\ \mathbf{b} &= \frac{1}{2\sqrt{Z_0}} (\mathbf{V} - Z_0 \mathbf{I}) = \frac{1}{2\sqrt{Z_0}} (\mathbf{Z} - Z_0 \mathbf{I}) \mathbf{I} \end{aligned} \quad (12.3.3)$$

where we used the impedance matrix relationship  $\mathbf{V} = \mathbf{Z}\mathbf{I}$  and defined the  $2 \times 2$  unit matrix  $\mathbf{I}$ . It follows then,

$$\frac{1}{2\sqrt{Z_0}} \mathbf{I} = (\mathbf{Z} + Z_0 \mathbf{I})^{-1} \mathbf{a} \Rightarrow \mathbf{b} = \frac{1}{2\sqrt{Z_0}} (\mathbf{Z} - Z_0 \mathbf{I}) \mathbf{I} = (\mathbf{Z} - Z_0 \mathbf{I}) (\mathbf{Z} + Z_0 \mathbf{I})^{-1} \mathbf{a}$$

Thus, the scattering matrix  $S$  will be related to the impedance matrix  $Z$  by

$$\boxed{S = (\mathbf{Z} - Z_0 \mathbf{I}) (\mathbf{Z} + Z_0 \mathbf{I})^{-1}} \Leftrightarrow \boxed{Z = (\mathbf{I} - S)^{-1} (\mathbf{I} + S) Z_0} \quad (12.3.4)$$

Explicitly, we have:

$$\begin{aligned} S &= \begin{bmatrix} Z_{11} - Z_0 & Z_{12} \\ Z_{21} & Z_{22} - Z_0 \end{bmatrix} \begin{bmatrix} Z_{11} + Z_0 & Z_{12} \\ Z_{21} & Z_{22} + Z_0 \end{bmatrix}^{-1} \\ &= \begin{bmatrix} Z_{11} - Z_0 & Z_{12} \\ Z_{21} & Z_{22} - Z_0 \end{bmatrix} \frac{1}{D_z} \begin{bmatrix} Z_{22} + Z_0 & -Z_{12} \\ -Z_{21} & Z_{11} + Z_0 \end{bmatrix} \end{aligned}$$

where  $D_z = \det(Z + Z_0 I) = (Z_{11} + Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}$ . Multiplying the matrix factors, we obtain:

$$S = \frac{1}{D_z} \begin{bmatrix} (Z_{11} - Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21} & 2Z_{12}Z_0 \\ 2Z_{21}Z_0 & (Z_{11} + Z_0)(Z_{22} - Z_0) - Z_{12}Z_{21} \end{bmatrix} \quad (12.3.5)$$

Similarly, the inverse relationship gives:

$$Z = \frac{Z_0}{D_s} \begin{bmatrix} (1 + S_{11})(1 - S_{22}) + S_{12}S_{21} & 2S_{12} \\ 2S_{21} & (1 - S_{11})(1 + S_{22}) + S_{12}S_{21} \end{bmatrix} \quad (12.3.6)$$

where  $D_s = \det(I - S) = (1 - S_{11})(1 - S_{22}) - S_{12}S_{21}$ . Expressing the impedance parameters in terms of the transfer matrix parameters, we also find:

$$S = \frac{1}{D_a} \begin{bmatrix} A + \frac{B}{Z_0} - CZ_0 - D & 2(AD - BC) \\ \frac{B}{Z_0} - CZ_0 + D & -A + \frac{B}{Z_0} \end{bmatrix} \quad (12.3.7)$$

where  $D_a = A + \frac{B}{Z_0} + CZ_0 + D$ .

## 12.4 Input and Output Reflection Coefficients

When the two-port is connected to a generator and load as in Fig. 12.1.4, the impedance and scattering matrix equations take the simpler forms:

$$\begin{aligned} \boxed{V_1 = Z_{in}I_1} & \quad \Leftrightarrow \quad \boxed{b_1 = \Gamma_{in}a_1} \\ \boxed{V_2 = Z_L I_2} & \quad \Leftrightarrow \quad \boxed{a_2 = \Gamma_L b_2} \end{aligned} \quad (12.4.1)$$

where  $Z_{in}$  is the input impedance at port 1, and  $\Gamma_{in}, \Gamma_L$  are the reflection coefficients at port 1 and at the load:

$$\Gamma_{in} = \frac{Z_{in} - Z_0}{Z_{in} + Z_0}, \quad \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad (12.4.2)$$

The input impedance and input reflection coefficient can be expressed in terms of the Z- and S-parameters, as follows:

$$\boxed{Z_{in} = Z_{11} - \frac{Z_{12}Z_{21}}{Z_{22} + Z_L}} \quad \Leftrightarrow \quad \boxed{\Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}} \quad (12.4.3)$$

The equivalence of these two expressions can be shown by using the parameter conversion formulas of Eqs. (12.3.5) and (12.3.6), or they can be shown indirectly, as follows. Starting with  $V_2 = Z_L I_2$  and using the second impedance matrix equation, we can solve for  $I_2$  in terms of  $I_1$ :

$$V_2 = Z_{21}I_1 - Z_{22}I_2 = Z_L I_2 \quad \Rightarrow \quad I_2 = \frac{Z_{21}}{Z_{22} + Z_L} I_1 \quad (12.4.4)$$

Then, the first impedance matrix equation implies:

$$V_1 = Z_{11}I_1 - Z_{12}I_2 = \left( Z_{11} - \frac{Z_{12}Z_{21}}{Z_{22} + Z_L} \right) I_1 = Z_{in}I_1$$

Starting again with  $V_2 = Z_L I_2$  we find for the traveling waves at port 2:

$$\begin{aligned} a_2 &= \frac{V_2 - Z_0 I_2}{2\sqrt{Z_0}} = \frac{Z_L - Z_0}{2\sqrt{Z_0}} I_2 \\ b_2 &= \frac{V_2 + Z_0 I_2}{2\sqrt{Z_0}} = \frac{Z_L + Z_0}{2\sqrt{Z_0}} I_2 \end{aligned} \quad \Rightarrow \quad \begin{aligned} a_2 &= \frac{Z_L - Z_0}{Z_L + Z_0} b_2 = \Gamma_L b_2 \\ b_2 &= \frac{Z_L + Z_0}{Z_L - Z_0} a_2 = \Gamma_{in} a_1 \end{aligned}$$

Using  $V_1 = Z_{in}I_1$ , a similar argument implies for the waves at port 1:

$$\begin{aligned} a_1 &= \frac{V_1 + Z_0 I_1}{2\sqrt{Z_0}} = \frac{Z_{in} + Z_0}{2\sqrt{Z_0}} I_1 \\ b_1 &= \frac{V_1 - Z_0 I_1}{2\sqrt{Z_0}} = \frac{Z_{in} - Z_0}{2\sqrt{Z_0}} I_1 \end{aligned} \quad \Rightarrow \quad \begin{aligned} b_1 &= \frac{Z_{in} - Z_0}{Z_{in} + Z_0} a_1 = \Gamma_{in} a_1 \\ a_1 &= \frac{Z_{in} + Z_0}{Z_{in} - Z_0} b_1 = \Gamma_{out} b_1 \end{aligned}$$

It follows then from the scattering matrix equations that:

$$b_2 = S_{21}a_1 + S_{22}a_2 = S_{22}a_1 + S_{22}\Gamma_L b_2 \quad \Rightarrow \quad \boxed{b_2 = \frac{S_{21}}{1 - S_{22}\Gamma_L} a_1} \quad (12.4.5)$$

which implies for  $b_1$ :

$$b_1 = S_{11}a_1 + S_{12}a_2 = S_{11}a_1 + S_{12}\Gamma_L b_2 = \left( S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \right) a_1 = \Gamma_{in} a_1$$

Reversing the roles of generator and load, we obtain the impedance and reflection coefficients from the output side of the two-port:

$$\boxed{Z_{out} = Z_{22} - \frac{Z_{12}Z_{21}}{Z_{11} + Z_G}} \quad \Leftrightarrow \quad \boxed{\Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_G}{1 - S_{11}\Gamma_G}} \quad (12.4.6)$$

where

$$\Gamma_{out} = \frac{Z_{out} - Z_0}{Z_{out} + Z_0}, \quad \Gamma_G = \frac{Z_G - Z_0}{Z_G + Z_0} \quad (12.4.7)$$

The input and output impedances allow one to replace the original two-port circuit of Fig. 12.1.4 by simpler equivalent circuits. For example, the two-port and the load can be replaced by the input impedance  $Z_{in}$  connected at port 1, as shown in Fig. 12.4.1.

 


Fig. 12.4.1 Input and output equivalent circuits.

Similarly, the generator and the two-port can be replaced by a Thévenin equivalent circuit connected at port 2. By determining the open-circuit voltage and short-circuit current at port 2, we find the corresponding Thévenin parameters in terms of the impedance parameters:

$$V_{\text{th}} = \frac{Z_{21}V_G}{Z_{11} + Z_G}, \quad Z_{\text{th}} = Z_{\text{out}} = Z_{22} - \frac{Z_{12}Z_{21}}{Z_{11} + Z_G} \quad (12.4.8)$$

## 12.5 Stability Circles

In discussing the stability conditions of a two-port in terms of  $S$ -parameters, the following definitions of constants are often used:

$$\begin{aligned} \Delta &= \det(S) = S_{11}S_{22} - S_{12}S_{21} \\ K &= \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|} && \text{(Rollett stability factor)} \\ \mu_1 &= \frac{1 - |S_{11}|^2}{|S_{22} - \Delta S_{11}^*| + |S_{12}S_{21}|} && \text{(Edwards-Sinsky stability parameter)} \\ \mu_2 &= \frac{1 - |S_{22}|^2}{|S_{11} - \Delta S_{22}^*| + |S_{12}S_{21}|} \\ B_1 &= 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ B_2 &= 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_1 &= S_{11} - \Delta S_{22}^*, \quad D_1 = |S_{11}|^2 - |\Delta|^2 \\ C_2 &= S_{22} - \Delta S_{11}^*, \quad D_2 = |S_{22}|^2 - |\Delta|^2 \end{aligned} \quad (12.5.1)$$

The quantity  $K$  is the Rollett stability factor [582], and  $\mu_1, \mu_2$ , the Edwards-Sinsky stability parameters [585]. The following identities hold among these constants:

$$\begin{aligned} B_1^2 - 4|C_1|^2 &= B_2^2 - 4|C_2|^2 = 4|S_{12}S_{21}|^2 (K^2 - 1) \\ |C_1|^2 &= |S_{12}S_{21}|^2 + (1 - |S_{22}|^2)D_1 \\ |C_2|^2 &= |S_{12}S_{21}|^2 + (1 - |S_{11}|^2)D_2 \end{aligned} \quad (12.5.2)$$

For example, noting that  $S_{12}S_{21} = S_{11}S_{22} - \Delta$ , the last of Eqs. (12.5.2) is a direct consequence of the identity:

$$|A - BC|^2 - |B - AC^*|^2 = (1 - |C|^2)(|A|^2 - |B|^2) \quad (12.5.3)$$

We define also the following parameters, which will be recognized as the centers and radii of the source and load stability circles:

$$c_G = \frac{C_1^*}{D_1}, \quad r_G = \frac{|S_{12}S_{21}|}{|D_1|} \quad \text{(source stability circle)} \quad (12.5.4)$$

$$c_L = \frac{C_2^*}{D_2}, \quad r_L = \frac{|S_{12}S_{21}|}{|D_2|} \quad \text{(load stability circle)} \quad (12.5.5)$$

They satisfy the following relationships, which are consequences of the last two of Eqs. (12.5.2) and the definitions (12.5.4) and (12.5.5):

$$\begin{aligned} 1 - |S_{11}|^2 &= (|c_L|^2 - r_L^2)D_2 \\ 1 - |S_{22}|^2 &= (|c_G|^2 - r_G^2)D_1 \end{aligned} \quad (12.5.6)$$

We note also that using Eqs. (12.5.6), the stability parameters  $\mu_1, \mu_2$  can be written as:

$$\begin{aligned} \mu_1 &= (|c_L| - r_L) \text{sign}(D_2) \\ \mu_2 &= (|c_G| - r_G) \text{sign}(D_1) \end{aligned} \quad (12.5.7)$$

For example, we have:

$$\mu_1 = \frac{1 - |S_{11}|^2}{|C_2| + |S_{12}S_{21}|} = \frac{D_2(|c_L|^2 - r_L^2)}{|D_2||c_L| + |D_2|r_L} = \frac{D_2(|c_L|^2 - r_L^2)}{|D_2|(|c_L| + r_L)} = \frac{D_2}{|D_2|}(|c_L| - r_L)$$

We finally note that the input and output reflection coefficients can be written in the alternative forms:

$$\begin{aligned} \Gamma_{\text{in}} &= S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} = \frac{S_{11} - \Delta\Gamma_L}{1 - S_{22}\Gamma_L} \\ \Gamma_{\text{out}} &= S_{22} + \frac{S_{12}S_{21}\Gamma_G}{1 - S_{22}\Gamma_G} = \frac{S_{22} - \Delta\Gamma_G}{1 - S_{11}\Gamma_G} \end{aligned} \quad (12.5.8)$$

Next, we discuss the stability conditions. The two-port is *unconditionally stable* if any generator and load impedances with positive resistive parts  $R_G, R_L$ , will always lead to input and output impedances with positive resistive parts  $R_{\text{in}}, R_{\text{out}}$ .

Equivalently, unconditional stability requires that any load and generator with  $|\Gamma_L| < 1$  and  $|\Gamma_G| < 1$  will result into  $|\Gamma_{\text{in}}| < 1$  and  $|\Gamma_{\text{out}}| < 1$ .

The two-port is termed *potentially or conditionally unstable* if there are  $|\Gamma_L| < 1$  and  $|\Gamma_G| < 1$  resulting into  $|\Gamma_{\text{in}}| \geq 1$  and/or  $|\Gamma_{\text{out}}| \geq 1$ .

The *load stability region* is the set of all  $\Gamma_L$  the result into  $|\Gamma_{\text{in}}| < 1$ , and the *source stability region*, the set of all  $\Gamma_G$  that result into  $|\Gamma_{\text{out}}| < 1$ .

In the unconditionally stable case, the load and source stability regions contain the entire unit-circles  $|\Gamma_L| < 1$  or  $|\Gamma_G| < 1$ . However, in the potentially unstable case, only

portions of the unit-circles may lie within the stability regions and such  $I_G$ ,  $I_L$  will lead to a stable input and output impedances.

The connection of the stability regions to the stability circles is brought about by the following identities, which can be proved easily using Eqs. (12.5.1)-(12.5.8):

$$\begin{aligned} 1 - |I_{in}|^2 &= \frac{|I_L - c_L|^2 - r_L^2 D_2}{|1 - S_{22} I_L|^2} \\ 1 - |I_{out}|^2 &= \frac{|I_G - c_G|^2 - r_G^2 D_1}{|1 - S_{11} I_G|^2} \end{aligned} \quad (12.5.9)$$

For example, the first can be shown starting with Eq. (12.5.8) and using the definitions (12.5.5) and the relationship (12.5.6):

$$\begin{aligned} 1 - |I_{in}|^2 &= 1 - \left| \frac{S_{11} - \Delta I_L}{1 - S_{22} I_L} \right|^2 = \frac{|S_{11} - \Delta I_L|^2 - |1 - S_{22} I_L|^2}{|1 - S_{22} I_L|^2} \\ &= \frac{(|S_{22}|^2 - |\Delta|^2) |I_L|^2 - (S_{22}^* - \Delta S_{11}^*) I_L - (S_{22}^* \Delta - \Delta^* S_{11}) I_L^* + 1 - |S_{11}|^2}{|1 - S_{22} I_L|^2} \\ &= \frac{D_2 |I_L|^2 - C_2 I_L - C_2^* I_L^* + 1 - |S_{11}|^2}{|1 - S_{22} I_L|^2} \\ &= \frac{D_2 (|I_L|^2 - c_L^* I_L - c_L I_L^* + |c_L|^2 - r_L^2)}{|1 - S_{22} I_L|^2} = \frac{D_2 (|I_L - c_L|^2 - r_L^2)}{|1 - S_{22} I_L|^2} \end{aligned}$$

It follows from Eq. (12.5.9) that the load stability region is defined by the conditions:

$$1 - |I_{in}|^2 > 0 \Leftrightarrow (|I_L - c_L|^2 - r_L^2) D_2 > 0$$

Depending on the sign of  $D_2$ , these are equivalent to the outside or the inside of the load stability circle of center  $c_L$  and radius  $r_L$ :

$$\begin{cases} |I_L - c_L| > r_L, & \text{if } D_2 > 0 \\ |I_L - c_L| < r_L, & \text{if } D_2 < 0 \end{cases} \quad (\text{load stability region}) \quad (12.5.10)$$

The boundary of the circle  $|I_L - c_L| = r_L$  corresponds to  $|I_{in}| = 1$ . The complement of these regions corresponds to the unstable region with  $|I_{in}| > 1$ . Similarly, we find for the source stability region:

$$\begin{cases} |I_G - c_G| > r_G, & \text{if } D_1 > 0 \\ |I_G - c_G| < r_G, & \text{if } D_1 < 0 \end{cases} \quad (\text{source stability region}) \quad (12.5.11)$$

In order to have unconditional stability, the stability regions must contain the unit-circle in its entirety. If  $D_2 > 0$ , the unit-circle and load stability circle must not overlap at all, as shown in Fig. 12.5.1. Geometrically, the distance between the points  $O$  and  $A$  in the figure is  $(OA) = |c_L| - r_L$ . The non-overlapping of the circles requires the condition  $(OA) > 1$ , or,  $|c_L| - r_L > 1$ .

If  $D_2 < 0$ , the stability region is the inside of the stability circle, and therefore, the unit-circle must lie within that circle. This requires that  $(OA) = r_L - |c_L| > 1$ , as shown in Fig. 12.5.1.

 


Fig. 12.5.1 Load stability regions in the unconditionally stable case.

These two conditions can be combined into  $\text{sign}(D_2) (|c_L| - r_L) > 1$ . But, that is equivalent to  $\mu_1 > 1$  according to Eq. (12.5.7). Geometrically, the parameter  $\mu_1$  represents the distance  $(OA)$ . Thus, the condition for the unconditional stability of the input is equivalent to:

$$\boxed{\mu_1 > 1} \quad (\text{unconditional stability condition}) \quad (12.5.12)$$

It has been shown by Edwards and Sinsky [585] that this single condition (or, alternatively, the single condition  $\mu_2 > 1$ ) is necessary and sufficient for the unconditional stability of both the input and output impedances of the two-port. Clearly, the source stability regions will be similar to those of Fig. 12.5.1.

If the stability condition is not satisfied, that is,  $\mu_1 < 1$ , then only that portion of the unit-circle that lies within the stability region will be stable and will lead to stable input and output impedances. Fig. 12.5.2 illustrates such a potentially unstable case.

 


Fig. 12.5.2 Load stability regions in potentially unstable case.

If  $D_2 > 0$ , then  $\mu_1 < 1$  is equivalent to  $|c_L| - r_L < 1$ , and if  $D_2 < 0$ , it is equivalent to  $r_L - |c_L| < 1$ . In either case, the unit-circle is partially overlapping with the stability



circle, as shown in Fig. 12.5.2. The portion of the unit-circle that does not lie within the stability region will correspond to an unstable  $Z_{in}$ .

There exist several other unconditional stability criteria that are equivalent to the single criterion  $\mu_1 > 1$ . They all require that the Rollett stability factor  $K$  be greater than unity,  $K > 1$ , as well as one other condition. Any one of the following criteria are necessary and sufficient for unconditional stability [583]:

$$\begin{aligned} K &> 1 \quad \text{and} \quad |\Delta| < 1 \\ K &> 1 \quad \text{and} \quad B_1 > 0 \\ K &> 1 \quad \text{and} \quad B_2 > 0 \\ K &> 1 \quad \text{and} \quad |S_{12}S_{21}| < 1 - |S_{11}|^2 \\ K &> 1 \quad \text{and} \quad |S_{12}S_{21}| < 1 - |S_{22}|^2 \end{aligned} \quad \text{(stability conditions)} \quad (12.5.13)$$

Their equivalence to  $\mu_1 > 1$  has been shown in [585]. In particular, it follows from the last two conditions that unconditional stability requires  $|S_{11}| < 1$  and  $|S_{22}| < 1$ . These are necessary but not sufficient for stability.

A very common circumstance in practice is to have a potentially unstable two-port, but with  $|S_{11}| < 1$  and  $|S_{22}| < 1$ . In such cases, Eq. (12.5.6) implies  $D_2(|c_L|^2 - r_L^2) > 0$ , and the lack of stability requires  $\mu_1 = \text{sign}(D_2)(|c_L|^2 - r_L^2) < 1$ .

Therefore, if  $D_2 > 0$ , then we must have  $|c_L|^2 - r_L^2 > 0$  and  $|c_L| - r_L < 1$ , which combine into the inequality  $r_L < |c_L| < r_L + 1$ . This is depicted in the left picture of Fig. 12.5.2. The geometrical distance ( $OA$ ) =  $|c_L| - r_L$  satisfies  $0 < (OA) < 1$ , so that stability circle partially overlaps with the unit-circle but does not enclose its center.

On the other hand, if  $D_2 < 0$ , the two conditions require  $|c_L|^2 - r_L^2 < 0$  and  $r_L - |c_L| < 1$ , which imply  $|c_L| < r_L < |c_L| + 1$ . This is depicted in the right Fig. 12.5.2. The geometrical distance ( $OA$ ) =  $r_L - |c_L|$  again satisfies  $0 < (OA) < 1$ , but now the center of the unit-circle lies within the stability circle, which is also the stability region.

We have written a number of MATLAB functions that facilitate working with  $S$ -parameters. They are described in detail later on:

```
smat      reshape S-parameters into S-matrix
sparam    calculate stability parameters
sgain     calculate transducer, available, operating, and unilateral power gains
smatch    calculate simultaneous conjugate match for generator and load
gin,gout  calculate input and output reflection coefficients
smith     draw a basic Smith chart
smithcir  draw a stability or gain circle on Smith chart
sgcirc    determine stability and gain circles
nfcirc    determine noise figure circles
nfig      calculate noise figure
```

The MATLAB function `sparam` calculates the stability parameters  $\mu_1, K, |\Delta|, B_1, B_2$ , as well as the parameters  $C_1, C_2, D_1, D_2$ . It has usage:

```
[K, mu, D, B1, B2, C1, C2, D1, D2] = sparam(S); % stability parameters
```

The function `sgcirc` calculates the centers and radii of the source and load stability circles. It also calculates gain circles to be discussed later on. Its usage is:

```
[cL, rL] = sgcirc(S, 'l'); % load or Zbin stability circle
[cG, rG] = sgcirc(S, 's'); % source or Zbout stability circle
```

The MATLAB function `smith` draws a basic Smith chart, and the function `smithcir` draws the stability circles:

```
smith(n); % draw four basic types of Smith charts, n = 1, 2, 3, 4
smith; % default Smith chart corresponding to n = 3
smithcir(c, r, max, width); % draw circle of center c and radius r
smithcir(c, r, max); % equivalent to linewidth=width=1
smithcir(c, r); % draw full circle with linewidth=width=1
```

The parameter `max` controls the portion of the stability circle that is visible outside the Smith chart. For example, `max = 1.1` will display only that portion of the circle that has  $|r| < 1.1$ .

**Example 12.5.1:** The Hewlett-Packard AT-41511 NPN bipolar transistor has the following  $S$ -parameters at 1 GHz and 2 GHz [854]:

$$\begin{aligned} S_{11} &= 0.48 \angle -149^\circ, & S_{21} &= 5.189 \angle 89^\circ, & S_{12} &= 0.073 \angle 43^\circ, & S_{22} &= 0.49 \angle -39^\circ \\ S_{11} &= 0.46 \angle 162^\circ, & S_{21} &= 2.774 \angle 59^\circ, & S_{12} &= 0.103 \angle 45^\circ, & S_{22} &= 0.42 \angle -47^\circ \end{aligned}$$

Determine the stability parameters, stability circles, and stability regions.

**Solution:** The transistor is potentially unstable at 1 GHz, but unconditionally stable at 2 GHz. The source and load stability circles at 1 GHz are shown in Fig. 12.5.3.

 


Fig. 12.5.3 Load and source stability circles at 1 GHz.

The MATLAB code used to generate this graph was:

```
S = smat([0.48 -149 5.189 89 0.073 43 0.49 -39]); % form S-matrix
[K, mu, D, B1, B2, C1, C2, D1, D2] = sparam(S); % stability parameters
[cL, rL] = sgcirc(S, 'l'); % stability circles
[cG, rG] = sgcirc(S, 's'); % stability circles
smith; % draw basic Smith chart
smithcir(cL, rL, 1.1, 1.5); % draw stability circles
smithcir(cG, rG, 1.1, 1.5); % draw stability circles
```

The computed stability parameters at 1 GHz were:

$$[K, \mu_1, |\Delta|, B_1, B_2, D_1, D_2] = [0.781, 0.847, 0.250, 0.928, 0.947, 0.168, 0.178]$$

The transistor is potentially unstable because  $K < 1$  even though  $|\Delta| < 1$ ,  $B_1 > 0$ , and  $B_2 > 0$ . The load and source stability circle centers and radii were:

$$c_L = 2.978 \angle 51.75^\circ, \quad r_L = 2.131$$

$$c_G = 3.098 \angle 162.24^\circ, \quad r_G = 2.254$$

Because both  $D_1$  and  $D_2$  are positive, both stability regions will be the portion of the Smith chart that lies outside the stability circles. For 2 GHz, we find:

$$[K, \mu_1, |\Delta|, B_1, B_2, D_1, D_2] = [1.089, 1.056, 0.103, 1.025, 0.954, 0.201, 0.166]$$

$$c_L = 2.779 \angle 50.12^\circ, \quad r_L = 1.723$$

$$c_G = 2.473 \angle -159.36^\circ, \quad r_G = 1.421$$

The transistor is stable at 2 GHz, with both load and source stability circles being completely outside the unit-circle.  $\square$

Problem 12.2 presents an example for which the  $D_2$  parameter is negative, so that the stability regions will be the insides of the stability circles. At one frequency, the unit-circle is partially overlapping with the stability circle, while at another frequency, it lies entirely within the stability circle.

## 12.6 Power Gains

The amplification (or attenuation) properties of the two-port can be deduced by comparing the power  $P_{\text{in}}$  going into the two-port to the power  $P_L$  coming out of the two-port and going into the load. These were given in Eq. (12.2.1) and we rewrite them as:

$$\begin{aligned} P_{\text{in}} &= \frac{1}{2} \operatorname{Re}[V_1^* I_1] = \frac{1}{2} R_{\text{in}} |I_1|^2 && \text{(power into two-port)} \\ P_L &= \frac{1}{2} \operatorname{Re}[V_2^* I_2] = \frac{1}{2} R_L |I_2|^2 && \text{(power out of two-port and into load)} \end{aligned} \quad (12.6.1)$$

where we used  $V_1 = Z_{\text{in}} I_1$ ,  $V_2 = Z_L I_2$ , and defined the real parts of the input and load impedances by  $R_{\text{in}} = \operatorname{Re}(Z_{\text{in}})$  and  $R_L = \operatorname{Re}(Z_L)$ . Using the equivalent circuits of Fig. 12.4.1, we may write  $I_1, I_2$  in terms of the generator voltage  $V_G$  and obtain:

$$\begin{aligned} P_{\text{in}} &= \frac{1}{2} \frac{|V_G|^2 R_{\text{in}}}{|Z_{\text{in}} + Z_G|^2} \\ P_L &= \frac{1}{2} \frac{|V_{\text{th}}|^2 R_L}{|Z_{\text{out}} + Z_L|^2} = \frac{1}{2} \frac{|V_G|^2 R_L |Z_{21}|^2}{|(Z_{11} + Z_G)(Z_{\text{out}} + Z_L)|^2} \end{aligned} \quad (12.6.2)$$

Using the identities of Problem 12.1,  $P_L$  can also be written in the alternative forms:

$$P_L = \frac{1}{2} \frac{|V_G|^2 R_L |Z_{21}|^2}{|(Z_{22} + Z_L)(Z_{\text{in}} + Z_G)|^2} = \frac{1}{2} \frac{|V_G|^2 R_L |Z_{21}|^2}{|(Z_{11} + Z_G)(Z_{22} + Z_L) - Z_{12} Z_{21}|^2} \quad (12.6.3)$$

The *maximum* power that can be delivered by the generator to a connected load is called the *available power* of the generator,  $P_{\text{avG}}$ , and is obtained when the load is conjugate-matched to the generator, that is,  $P_{\text{avG}} = P_{\text{in}}$  when  $Z_{\text{in}} = Z_G^*$ .

Similarly, the *available* power from the two-port network,  $P_{\text{avN}}$ , is the maximum power that can be delivered by the Thévenin-equivalent circuit of Fig. 12.4.1 to a connected load, that is,  $P_{\text{avN}} = P_L$  when  $Z_L = Z_{\text{th}}^* = Z_{\text{out}}^*$ . It follows then from Eq. (12.6.2) that the available powers will be:

$$P_{\text{avG}} = \max P_{\text{in}} = \frac{|V_G|^2}{8R_G} \quad \text{(available power from generator)} \quad (12.6.4)$$

$$P_{\text{avN}} = \max P_L = \frac{|V_{\text{th}}|^2}{8R_{\text{out}}} \quad \text{(available power from network)}$$

Using Eq. (12.4.8),  $P_{\text{avN}}$  can also be written as:

$$P_{\text{avN}} = \frac{|V_G|^2}{8R_{\text{out}}} \left| \frac{Z_{21}}{Z_{11} + Z_G} \right|^2 \quad (12.6.5)$$

The powers can be expressed completely in terms of the  $S$ -parameters of the two-port and the input and output reflection coefficients. With the help of the identities of Problem 12.1, we find the alternative expressions for  $P_{\text{in}}$  and  $P_L$ :

$$\begin{aligned} P_{\text{in}} &= \frac{|V_G|^2}{8Z_0} \frac{(1 - |\Gamma_{\text{in}}|^2) |1 - \Gamma_G|^2}{|1 - \Gamma_{\text{in}} \Gamma_G|^2} \\ P_L &= \frac{|V_G|^2}{8Z_0} \frac{(1 - |\Gamma_L|^2) |1 - \Gamma_G|^2 |S_{21}|^2}{|(1 - \Gamma_{\text{in}} \Gamma_G)(1 - S_{22} \Gamma_L)|^2} \\ &= \frac{|V_G|^2}{8Z_0} \frac{(1 - |\Gamma_L|^2) |1 - \Gamma_G|^2 |S_{21}|^2}{|(1 - \Gamma_{\text{out}} \Gamma_L)(1 - S_{11} \Gamma_G)|^2} \\ &= \frac{|V_G|^2}{8Z_0} \frac{(1 - |\Gamma_L|^2) |1 - \Gamma_G|^2 |S_{21}|^2}{|(1 - S_{11} \Gamma_G)(1 - S_{22} \Gamma_L) - S_{12} S_{21} \Gamma_G \Gamma_L|^2} \end{aligned} \quad (12.6.6)$$

Similarly, we have for  $P_{\text{avG}}$  and  $P_{\text{avN}}$ :

$$\begin{aligned} P_{\text{avG}} &= \frac{|V_G|^2}{8Z_0} \frac{|1 - \Gamma_G|^2}{|1 - |\Gamma_G|^2|} \\ P_{\text{avN}} &= \frac{|V_G|^2}{8Z_0} \frac{|1 - \Gamma_G|^2 |S_{21}|^2}{(1 - |\Gamma_{\text{out}}|^2) |1 - S_{11} \Gamma_G|^2} \end{aligned} \quad (12.6.7)$$

It is evident that  $P_{\text{avG}}, P_{\text{avN}}$  are obtained from  $P_{\text{in}}, P_L$  by setting  $\Gamma_{\text{in}} = \Gamma_G^*$  and  $\Gamma_L = \Gamma_G^*$ , which are equivalent to the conjugate-match conditions.



Three widely used definitions for the *power gain* of the two-port network are the *transducer* power gain  $G_T$ , the *available* power gain  $G_a$ , and the power gain  $G_p$ , also called the operating gain. They are defined as follows:

$$\begin{aligned} G_T &= \frac{\text{power out of network}}{\text{maximum power in}} = \frac{P_L}{P_{\text{avG}}} && \text{(transducer power gain)} \\ G_a &= \frac{\text{maximum power out}}{\text{maximum power in}} = \frac{P_{\text{avN}}}{P_{\text{avG}}} && \text{(available power gain)} \\ G_p &= \frac{\text{power out of network}}{\text{power into network}} = \frac{P_L}{P_{\text{in}}} && \text{(operating power gain)} \end{aligned} \quad (12.6.8)$$

Each gain is expressible either in terms of the  $Z$ -parameters of the two-port, or in terms of its  $S$ -parameters. In terms of  $Z$ -parameters, the transducer gain is given by the following forms, obtained from the three forms of  $P_L$  in Eqs. (12.6.2) and (12.6.3):

$$\begin{aligned} G_T &= \frac{4R_G R_L |Z_{21}|^2}{|(Z_{22} + Z_L)(Z_{\text{in}} + Z_G)|^2} \\ &= \frac{4R_G R_L |Z_{21}|^2}{|(Z_{11} + Z_G)(Z_{\text{out}} + Z_L)|^2} \\ &= \frac{4R_G R_L |Z_{21}|^2}{|(Z_{11} + Z_G)(Z_{22} + Z_L) - Z_{12}Z_{21}|^2} \end{aligned} \quad (12.6.9)$$

And, in terms of the  $S$ -parameters:

$$\begin{aligned} G_T &= \frac{1 - |I_G|^2}{|1 - I_{\text{in}} I_G|^2} |S_{21}|^2 \frac{1 - |I_L|^2}{|1 - S_{22} I_L|^2} \\ &= \frac{1 - |I_G|^2}{|1 - S_{11} I_G|^2} |S_{21}|^2 \frac{1 - |I_L|^2}{|1 - I_{\text{out}} I_L|^2} \\ &= \frac{(1 - |I_G|^2) |S_{21}|^2 (1 - |I_L|^2)}{|(1 - S_{11} I_G)(1 - S_{22} I_L) - S_{12} S_{21} I_G I_L|^2} \end{aligned} \quad (12.6.10)$$

Similarly, we have for  $G_a$  and  $G_p$ :

$$\begin{aligned} G_a &= \frac{R_G}{R_{\text{out}}} \left| \frac{Z_{21}}{Z_{11} + Z_G} \right|^2 = \frac{1 - |I_G|^2}{|1 - S_{11} I_G|^2} |S_{21}|^2 \frac{1}{1 - |I_{\text{out}}|^2} \\ G_p &= \frac{R_L}{R_{\text{in}}} \left| \frac{Z_{21}}{Z_{22} + Z_L} \right|^2 = \frac{1}{1 - |I_{\text{in}}|^2} |S_{21}|^2 \frac{1 - |I_L|^2}{|1 - S_{22} I_L|^2} \end{aligned} \quad (12.6.11)$$

The transducer gain  $G_T$  is, perhaps, the most representative measure of gain for the two-port because it incorporates the effects of both the load and generator impedances, whereas  $G_a$  depends only on the generator impedance and  $G_p$  only on the load impedance.

If the generator and load impedances are matched to the reference impedance  $Z_0$ , so that  $Z_G = Z_L = Z_0$  and  $I_G = I_L = 0$ , and  $I_{\text{in}} = S_{11}$ ,  $I_{\text{out}} = S_{22}$ , then the power gains reduce to:

$$G_T = |S_{21}|^2, \quad G_a = \frac{|S_{21}|^2}{1 - |S_{22}|^2}, \quad G_p = \frac{|S_{21}|^2}{1 - |S_{11}|^2} \quad (12.6.12)$$

A *unilateral* two-port has by definition zero reverse transmission coefficient, that is,  $S_{12} = 0$ . In this case, the input and output reflection coefficients simplify into:

$$I_{\text{in}} = S_{11}, \quad I_{\text{out}} = S_{22} \quad \text{(unilateral two-port)} \quad (12.6.13)$$

The expressions of the power gains simplify somewhat in this case:

$$\begin{aligned} G_{Tu} &= \frac{1 - |I_G|^2}{|1 - S_{11} I_G|^2} |S_{21}|^2 \frac{1 - |I_L|^2}{|1 - S_{22} I_L|^2} \\ G_{au} &= \frac{1 - |I_G|^2}{|1 - S_{11} I_G|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2} && \text{(unilateral gains)} \\ G_{pu} &= \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1 - |I_L|^2}{|1 - S_{22} I_L|^2} \end{aligned} \quad (12.6.14)$$

For both the bilateral and unilateral cases, the gains  $G_a$ ,  $G_p$  are obtainable from  $G_T$  by setting  $I_L = I_{\text{out}}^*$  and  $I_{\text{in}} = I_G^*$ , respectively, as was the case for  $P_{\text{avN}}$  and  $P_{\text{avG}}$ .

The relative power ratios  $P_{\text{in}}/P_{\text{avG}}$  and  $P_L/P_{\text{avN}}$  measure the mismatching between the generator and the two-port and between the load and the two-port. Using the definitions for the power gains, we obtain the input and output *mismatch factors*:

$$M_{\text{in}} = \frac{P_{\text{in}}}{P_{\text{avG}}} = \frac{G_T}{G_p} = \frac{4R_{\text{in}} R_G}{|Z_{\text{in}} + Z_G|^2} = \frac{(1 - |I_{\text{in}}|^2)(1 - |I_G|^2)}{|1 - I_{\text{in}} I_G|^2} \quad (12.6.15)$$

$$M_{\text{out}} = \frac{P_L}{P_{\text{avN}}} = \frac{G_T}{G_a} = \frac{4R_{\text{out}} R_L}{|Z_{\text{out}} + Z_L|^2} = \frac{(1 - |I_{\text{out}}|^2)(1 - |I_L|^2)}{|1 - I_{\text{out}} I_L|^2} \quad (12.6.16)$$

The mismatch factors are always less than or equal to unity (for positive  $R_{\text{in}}$  and  $R_{\text{out}}$ .) Clearly,  $M_{\text{in}} = 1$  under the conjugate-match condition  $Z_{\text{in}} = Z_G^*$  or  $I_{\text{in}} = I_G^*$ , and  $M_{\text{out}} = 1$  if  $Z_L = Z_{\text{out}}^*$  or  $I_L = I_{\text{out}}^*$ . The mismatch factors can also be written in the following forms, which show more explicitly the mismatch properties:

$$M_{\text{in}} = 1 - \left| \frac{I_{\text{in}} - I_G^*}{1 - I_{\text{in}} I_G} \right|^2, \quad M_{\text{out}} = 1 - \left| \frac{I_{\text{out}} - I_L^*}{1 - I_{\text{out}} I_L} \right|^2 \quad (12.6.17)$$

These follow from the identity:

$$|1 - \Gamma_1 \Gamma_2|^2 - |I_1 - I_2^*|^2 = (1 - |\Gamma_1|^2)(1 - |\Gamma_2|^2) \quad (12.6.18)$$

The transducer gain is *maximized* when the two-port is *simultaneously* conjugate matched, that is, when  $I_{\text{in}} = I_G^*$  and  $I_L = I_{\text{out}}^*$ . Then,  $M_{\text{in}} = M_{\text{out}} = 1$  and the three gains become equal. The common maximum gain achieved by simultaneous matching is called the *maximum available gain* (MAG):

$$G_{T,\text{max}} = G_{a,\text{max}} = G_{p,\text{max}} = G_{\text{MAG}} \quad (12.6.19)$$

Simultaneous matching is discussed in Sec. 12.8. The necessary and sufficient condition for simultaneous matching is  $K \geq 1$ , where  $K$  is the Rollett stability factor. It can be shown that the MAG can be expressed as:

$$G_{\text{MAG}} = \frac{|S_{21}|}{|S_{12}|} (K - \sqrt{K^2 - 1}) \quad (\text{maximum available gain}) \quad (12.6.20)$$

The *maximum stable gain* (MSG) is the maximum value  $G_{\text{MAG}}$  can have, which is achievable when  $K = 1$ :

$$G_{\text{MSG}} = \frac{|S_{21}|}{|S_{12}|} \quad (\text{maximum stable gain}) \quad (12.6.21)$$

In the unilateral case, the MAG is obtained either by setting  $I_G = I_{\text{in}}^* = S_{11}^*$  and  $I_L = I_{\text{out}}^* = S_{22}^*$  in Eq. (12.6.14), or by a careful limiting process in Eq. (12.6.20), in which  $K \rightarrow \infty$  so that both the numerator factor  $K - \sqrt{K^2 - 1}$  and the denominator factor  $|S_{12}|$  tend to zero. With either method, we find the unilateral MAG:

$$G_{\text{MAG},u} = \frac{|S_{21}|^2}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)} = G_1 |S_{21}|^2 G_2 \quad (\text{unilateral MAG}) \quad (12.6.22)$$

The maximum unilateral input and output gain factors are:

$$G_1 = \frac{1}{1 - |S_{11}|^2}, \quad G_2 = \frac{1}{1 - |S_{22}|^2} \quad (12.6.23)$$

They are the maxima of the input and output gain factors in Eq. (12.6.14) realized with conjugate matching, that is, with  $I_G = S_{11}^*$  and  $I_L = S_{22}^*$ . For any other values of the reflection coefficients (such that  $|I_G| < 1$  and  $|I_L| < 1$ ), we have the following inequalities, which follow from the identity (12.6.18):

$$\frac{1 - |I_G|^2}{|1 - S_{11}I_G|^2} \leq \frac{1}{1 - |S_{11}|^2}, \quad \frac{1 - |I_L|^2}{|1 - S_{22}I_L|^2} \leq \frac{1}{1 - |S_{22}|^2} \quad (12.6.24)$$

Often two-ports, such as most microwave transistor amplifiers, are approximately unilateral, that is, the measured  $S$ -parameters satisfy  $|S_{12}| \ll |S_{21}|$ . To decide whether the two-port should be treated as unilateral, a figure of merit is used, which is essentially the comparison of the maximum unilateral gain to the transducer gain of the actual device under the same matching conditions, that is,  $I_G = S_{11}^*$  and  $I_L = S_{22}^*$ .

For these matched values of  $I_G, I_L$ , the ratio of the bilateral and unilateral transducer gains can be shown to have the form:

$$g_u = \frac{G_T}{G_{Tu}} = \frac{1}{|1 - U|^2}, \quad U = \frac{S_{12}S_{21}S_{11}^*S_{22}^*}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)} \quad (12.6.25)$$

The quantity  $|U|$  is known as the *unilateral figure of merit*. If the relative gain ratio  $g_u$  is near unity (typically, within 10 percent of unity), the two-port may be treated as unilateral.

The MATLAB function `sgain` computes the transducer, available, and operating power gains, given the  $S$ -parameters and the reflection coefficients  $I_G, I_L$ . In addition,

it computes the unilateral gains, the maximum available gain, and the maximum stable gain. It also computes the unilateral figure of merit ratio (12.6.25). It has usage:

```
Gt = sgain(S,gG,gL);      % transducer power gain at given ΓbG, ΓbL
Ga = sgain(S,gG,'a');    % available power gain at given ΓbG with ΓbL = Γbout*
Gp = sgain(S,gL,'p');    % operating power gain at given ΓbL with ΓbG = Γbin*

Gmag = sgain(S);        % maximum available gain (MAG)
Gmsg = sgain(S,'msg');  % maximum stable gain (MSG)

Gu = sgain(S,'u');      % maximum unilateral gain, Eq. (12.6.22)
G1 = sgain(S,'u1');     % maximum unilateral input gain, Eq. (12.6.23)
G2 = sgain(S,'u2');     % maximum unilateral output gain, Eq. (12.6.23)
gu = sgain(S,'ufm');    % unilateral figure of merit gain ratio, Eq. (12.6.25)
```

The MATLAB functions `gin` and `gout` compute the input and output reflection coefficients from  $S$  and  $I_G, I_L$ . They have usage:

```
Gin = gin(S,gL);        % input reflection coefficient, Eq. (12.4.3)
Gout = gout(S,gG);     % output reflection coefficient, Eq. (12.4.6)
```

**Example 12.6.1:** A microwave transistor amplifier uses the Hewlett-Packard AT-41410 NPN bipolar transistor with the following  $S$ -parameters at 2 GHz [854]:

$$S_{11} = 0.61 \angle 165^\circ, \quad S_{21} = 3.72 \angle 59^\circ, \quad S_{12} = 0.05 \angle 42^\circ, \quad S_{22} = 0.45 \angle -48^\circ$$

Calculate the input and output reflection coefficients and the various power gains, if the amplifier is connected to a generator and load with impedances  $Z_G = 10 - 20j$  and  $Z_L = 30 + 40j$  ohm.

**Solution:** The following MATLAB code will calculate all the required gains:

```
Z0 = 50;                % normalization impedance
ZG = 10+20j;           % ΓbG = -0.50 + 0.50j = 0.71 ∠ 135°
ZL = 30-40j;           % ΓbL = -0.41 - 0.43j = 0.59 ∠ -133.15°

S = smat([0.61 165 3.72 59 0.05 42 0.45 -48]); % reshape S into matrix

Gin = gin(S,gL);       % Γbin = 0.54 ∠ 162.30°
Gout = gout(S,gG);     % Γbout = 0.45 ∠ -67.46°

Gt = sgain(S,gG,gL);   % GbT = 4.71, or, 6.73 dB
Ga = sgain(S,gG,'a'); % Gba = 11.44, or, 10.58 dB
Gp = sgain(S,gL,'p'); % Gbp = 10.51, or, 10.22 dB

Gu = sgain(S,'u');     % Gbu = 27.64, or, 14.41 dB
G1 = sgain(S,'u1');    % Gb1 = 1.59, or, 2.02 dB
G2 = sgain(S,'u2');    % Gb2 = 1.25, or, 0.98 dB
gu = sgain(S,'ufm');   % gbu = 1.23, or, 0.89 dB

Gmag = sgain(S);       % GbMAG = 41.50, or, 16.18 dB
Gmsg = sgain(S,'msg'); % GbMSG = 74.40, or, 18.72 dB
```

The amplifier cannot be considered to be unilateral as the unilateral figure of merit ratio  $g_M = 1.23$  is fairly large (larger than 10 percent from unity.)

The amplifier is operating at a gain of  $G_T = 6.73$  dB, which is far from the maximum value of  $G_{\text{MAG}} = 16.18$  dB. This is because it is mismatched with the given generator and load impedances.

To realize the optimum gain  $G_{\text{MAG}}$  the amplifier must 'see' certain optimum generator and load impedances or reflection coefficients. These can be calculated by the MATLAB function `smatch` and are found to be:

$$\begin{aligned} \Gamma_G &= 0.82 \angle -162.67^\circ & \Rightarrow & Z_G = g2z(Z_G, Z_0) = 5.12 - 7.54j \Omega \\ \Gamma_L &= 0.75 \angle 52.57^\circ & \Rightarrow & Z_L = g2z(Z_L, Z_0) = 33.66 + 91.48j \Omega \end{aligned}$$

The design of such optimum matching terminations and the function `smatch` are discussed in Sec. 12.8. The functions `g2z` and `z2g` were discussed in Sec. 9.7.  $\square$

## 12.7 Generalized S-Parameters and Power Waves

The practical usefulness of the S-parameters lies in the fact that the definitions (12.1.4) represent forward and backward traveling waves, which can be measured remotely by connecting a network analyzer to the two-port with transmission lines of characteristic impedance equal to the normalization impedance  $Z_0$ . This was depicted in Fig. 12.1.3.

A generalized definition of S-parameters and wave variables can be given by using in Eq. (12.1.4) two different normalization impedances for the input and output ports. Anticipating that the two-port will be connected to a generator and load of impedances  $Z_G$  and  $Z_L$ , a particularly convenient choice is to use  $Z_G$  for the input normalization impedance and  $Z_L$  for the output one, leading to the definition of the *power waves* (as opposed to traveling waves) [573–575, 577]:

$$\begin{aligned} a'_1 &= \frac{V_1 + Z_G I_1}{2\sqrt{R_G}} & a'_2 &= \frac{V_2 - Z_L I_2}{2\sqrt{R_L}} \\ b'_1 &= \frac{V_1 - Z_G^* I_1}{2\sqrt{R_G}} & b'_2 &= \frac{V_2 + Z_L^* I_2}{2\sqrt{R_L}} \end{aligned} \quad \text{(power waves)} \quad (12.7.1)$$

We note that the  $b$ -waves involve the complex-conjugates of the impedances. The quantities  $R_G, R_L$  are the resistive parts of  $Z_G, Z_L$  and are assumed to be positive. These definitions reduce to the conventional traveling ones if  $Z_G = Z_L = Z_0$ .

These "wave" variables can no longer be interpreted as incoming and outgoing waves from the two sides of the two-port. However, as we see below, they have a nice interpretation in terms of power transfer to and from the two-port and simplify the expressions for the power gains. Inverting Eqs. (12.7.1), we have:

$$\begin{aligned} V_1 &= \frac{1}{\sqrt{R_G}} (Z_G^* a'_1 + Z_G b'_1) & V_2 &= \frac{1}{\sqrt{R_L}} (Z_L^* a'_2 + Z_L b'_2) \\ I_1 &= \frac{1}{\sqrt{R_G}} (a'_1 - b'_1) & I_2 &= \frac{1}{\sqrt{R_L}} (b'_2 - a'_2) \end{aligned} \quad (12.7.2)$$

The power waves can be related directly to the traveling waves. For example, expressing Eqs. (12.7.1) and (12.1.5) in matrix form, we have for port-1:

$$\begin{bmatrix} a'_1 \\ b'_1 \end{bmatrix} = \frac{1}{2\sqrt{R_G}} \begin{bmatrix} 1 & Z_G \\ 1 & -Z_G^* \end{bmatrix} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}, \quad \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \frac{1}{\sqrt{Z_0}} \begin{bmatrix} Z_0 & Z_0 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} a_1 \\ b_1 \end{bmatrix}$$

It follows that:

$$\begin{aligned} \begin{bmatrix} a'_1 \\ b'_1 \end{bmatrix} &= \frac{1}{2\sqrt{R_G Z_0}} \begin{bmatrix} 1 & Z_G \\ 1 & -Z_G^* \end{bmatrix} \begin{bmatrix} Z_0 & Z_0 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} a_1 \\ b_1 \end{bmatrix} \quad \text{or,} \\ \begin{bmatrix} a'_1 \\ b'_1 \end{bmatrix} &= \frac{1}{2\sqrt{R_G Z_0}} \begin{bmatrix} Z_0 + Z_G & Z_0 - Z_G \\ Z_0 - Z_G^* & Z_0 + Z_G^* \end{bmatrix} \begin{bmatrix} a_1 \\ b_1 \end{bmatrix} \end{aligned} \quad (12.7.3)$$

The entries of this matrix can be expressed directly in terms of the reflection coefficient  $\Gamma_G$ . Using the identities of Problem 12.3, we may rewrite Eq. (12.7.3) and its inverse as follows:

$$\begin{aligned} \begin{bmatrix} a'_1 \\ b'_1 \end{bmatrix} &= \frac{1}{\sqrt{1 - |\Gamma_G|^2}} \begin{bmatrix} e^{j\phi_G} & -\Gamma_G e^{j\phi_G} \\ -\Gamma_G^* e^{-j\phi_G} & e^{-j\phi_G} \end{bmatrix} \begin{bmatrix} a_1 \\ b_1 \end{bmatrix} \\ \begin{bmatrix} a_1 \\ b_1 \end{bmatrix} &= \frac{1}{\sqrt{1 - |\Gamma_G|^2}} \begin{bmatrix} e^{-j\phi_G} & \Gamma_G e^{j\phi_G} \\ \Gamma_G^* e^{-j\phi_G} & e^{j\phi_G} \end{bmatrix} \begin{bmatrix} a'_1 \\ b'_1 \end{bmatrix} \end{aligned} \quad (12.7.4)$$

where, noting that the quantity  $|1 - \Gamma_G|/(1 - \Gamma_G)$  is a pure phase factor, we defined:

$$\Gamma_G = \frac{Z_G - Z_0}{Z_G + Z_0}, \quad e^{j\phi_G} = \frac{|1 - \Gamma_G|}{1 - \Gamma_G} = \frac{1 - \Gamma_G^*}{|1 - \Gamma_G|} \quad (12.7.5)$$

Similarly, we have for the power and traveling waves at port-2:

$$\begin{aligned} \begin{bmatrix} a'_2 \\ b'_2 \end{bmatrix} &= \frac{1}{\sqrt{1 - |\Gamma_L|^2}} \begin{bmatrix} e^{j\phi_L} & -\Gamma_L e^{j\phi_L} \\ -\Gamma_L^* e^{-j\phi_L} & e^{-j\phi_L} \end{bmatrix} \begin{bmatrix} a_2 \\ b_2 \end{bmatrix} \\ \begin{bmatrix} a_2 \\ b_2 \end{bmatrix} &= \frac{1}{\sqrt{1 - |\Gamma_L|^2}} \begin{bmatrix} e^{-j\phi_L} & \Gamma_L e^{j\phi_L} \\ \Gamma_L^* e^{-j\phi_L} & e^{j\phi_L} \end{bmatrix} \begin{bmatrix} a'_2 \\ b'_2 \end{bmatrix} \end{aligned} \quad (12.7.6)$$

where

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}, \quad e^{j\phi_L} = \frac{|1 - \Gamma_L|}{1 - \Gamma_L} = \frac{1 - \Gamma_L^*}{|1 - \Gamma_L|} \quad (12.7.7)$$

The generalized S-parameters are the scattering parameters with respect to the power wave variables, that is,

$$\begin{bmatrix} b'_1 \\ b'_2 \end{bmatrix} = \begin{bmatrix} S'_{11} & S'_{12} \\ S'_{21} & S'_{22} \end{bmatrix} \begin{bmatrix} a'_1 \\ a'_2 \end{bmatrix} \Rightarrow \mathbf{b}' = \mathbf{S}' \mathbf{a}' \quad (12.7.8)$$

To relate  $\mathbf{S}'$  to the conventional scattering matrix  $\mathbf{S}$ , we define the following diagonal matrices:

$$\Gamma = \begin{bmatrix} \Gamma_G & 0 \\ 0 & \Gamma_L \end{bmatrix}, \quad F = \begin{bmatrix} \frac{e^{j\phi_G}}{\sqrt{1-|\Gamma_G|^2}} & 0 \\ 0 & \frac{e^{j\phi_L}}{\sqrt{1-|\Gamma_L|^2}} \end{bmatrix} = \begin{bmatrix} F_G & 0 \\ 0 & F_L \end{bmatrix} \quad (12.7.9)$$

Using these matrices, it follows from Eqs. (12.7.4) and (12.7.6):

$$a'_1 = F_G(a_1 - \Gamma_G b_1) \Rightarrow \mathbf{a}' = F(\mathbf{a} - \Gamma \mathbf{b}) \quad (12.7.10)$$

$$a'_2 = F_L(a_2 - \Gamma_L b_2)$$

$$b'_1 = F_G^*(b_1 - \Gamma_G^* a_1) \Rightarrow \mathbf{b}' = F^*(\mathbf{b} - \Gamma^* \mathbf{a}) \quad (12.7.11)$$

$$b'_2 = F_L^*(b_2 - \Gamma_L^* a_2)$$

Using  $\mathbf{b} = \mathbf{S}\mathbf{a}$ , we find

$$\mathbf{a}' = F(\mathbf{a} - \Gamma \mathbf{b}) = F(I - \Gamma S)\mathbf{a} \Rightarrow \mathbf{a} = (I - \Gamma S)^{-1} F^{-1} \mathbf{a}'$$

$$\mathbf{b}' = F^*(S - \Gamma^* \mathbf{a}) = F^*(S - \Gamma^*) (I - \Gamma S)^{-1} F^{-1} \mathbf{a}' = S' \mathbf{a}'$$

where  $I$  is the  $2 \times 2$  unit matrix. Thus, the generalized S-matrix is:

$$\boxed{S' = F^*(S - \Gamma^*) (I - \Gamma S)^{-1} F^{-1}} \quad (12.7.12)$$

We note that  $S' = S$  when  $Z_G = Z_L = Z_0$ , that is, when  $\Gamma_G = \Gamma_L = 0$ . The explicit expressions for the matrix elements of  $S'$  can be derived as follows:

$$S'_{11} = \frac{(S_{11} - \Gamma_G^*)(1 - S_{22}\Gamma_L) + S_{21}S_{12}\Gamma_L}{(1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_G\Gamma_L} e^{-2j\phi_G} \quad (12.7.13a)$$

$$S'_{22} = \frac{(S_{22} - \Gamma_L^*)(1 - S_{11}\Gamma_G) + S_{21}S_{12}\Gamma_G}{(1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_G\Gamma_L} e^{-2j\phi_L}$$

$$S'_{21} = \frac{\sqrt{1-|\Gamma_G|^2} S_{21} \sqrt{1-|\Gamma_L|^2}}{(1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_G\Gamma_L} e^{-j(\phi_G + \phi_L)} \quad (12.7.13b)$$

$$S'_{12} = \frac{\sqrt{1-|\Gamma_L|^2} S_{12} \sqrt{1-|\Gamma_G|^2}}{(1 - S_{11}\Gamma_G)(1 - S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_G\Gamma_L} e^{-j(\phi_L + \phi_G)}$$

The  $S'_{11}, S'_{22}$  parameters can be rewritten in terms of the input and output reflection coefficients by using Eq. (12.13.2) and the following factorization identities:

$$(S_{11} - \Gamma_G^*)(1 - S_{22}\Gamma_L) + S_{21}S_{12}\Gamma_L = (I_{\text{in}} - \Gamma_G^*)(1 - S_{22}\Gamma_L)$$

$$(S_{22} - \Gamma_L^*)(1 - S_{11}\Gamma_G) + S_{21}S_{12}\Gamma_G = (I_{\text{out}} - \Gamma_L^*)(1 - S_{11}\Gamma_G)$$

It then follows from Eq. (12.7.13) that:

$$S'_{11} = \frac{I_{\text{in}} - \Gamma_G^*}{1 - I_{\text{in}}\Gamma_G} e^{-2j\phi_G}, \quad S'_{22} = \frac{I_{\text{out}} - \Gamma_L^*}{1 - I_{\text{out}}\Gamma_L} e^{-2j\phi_L} \quad (12.7.14)$$

Therefore, the mismatch factors (12.6.17) are recognized to be:

$$M_G = 1 - |S'_{11}|^2, \quad M_L = 1 - |S'_{22}|^2 \quad (12.7.15)$$

The power flow relations (12.2.1) into and out of the two-port are also valid in terms of the power wave variables. Using Eq. (12.7.2), it can be shown that:

$$P_{\text{in}} = \frac{1}{2} \text{Re}[V_1^* I_1] = \frac{1}{2} |a'_1|^2 - \frac{1}{2} |b'_1|^2 \quad (12.7.16)$$

$$P_L = \frac{1}{2} \text{Re}[V_2^* I_2] = \frac{1}{2} |b'_2|^2 - \frac{1}{2} |a'_2|^2$$

In the definitions (12.7.1), the impedances  $Z_G, Z_L$  are arbitrary normalization parameters. However, if the two-port is actually connected to a generator  $V_G$  with impedance  $Z_G$  and a load  $Z_L$ , then the power waves take particularly simple forms.

It follows from Fig. 12.1.4 that  $V_G = V_1 + Z_G I_1$  and  $V_2 = Z_L I_2$ . Therefore, definitions Eq. (12.7.1) give:

$$a'_1 = \frac{V_1 + Z_G I_1}{2\sqrt{R_G}} = \frac{V_G}{2\sqrt{R_G}}$$

$$a'_2 = \frac{V_2 - Z_L I_2}{2\sqrt{R_L}} = 0 \quad (12.7.17)$$

$$b'_2 = \frac{V_2 + Z_L^* I_2}{2\sqrt{R_L}} = \frac{Z_L + Z_L^*}{2\sqrt{R_L}} I_2 = \frac{2R_L}{2\sqrt{R_L}} I_2 = \sqrt{R_L} I_2$$

It follows that the available power from the generator and the power delivered to the load are given simply by:

$$P_{\text{avg}} = \frac{|V_G|^2}{8R_G} = \frac{1}{2} |a'_1|^2 \quad (12.7.18)$$

$$P_L = \frac{1}{2} R_L |I_2|^2 = \frac{1}{2} |b'_2|^2$$

Because  $a'_2 = 0$ , the generalized scattering matrix gives,  $b'_1 = S'_{11} a'_1$  and  $b'_2 = S'_{21} a'_1$ . The power expressions (12.7.16) then become:

$$P_{\text{in}} = \frac{1}{2} |a'_1|^2 - \frac{1}{2} |b'_1|^2 = (1 - |S'_{11}|^2) \frac{1}{2} |a'_1|^2 = (1 - |S'_{11}|^2) P_{\text{avg}}$$

$$P_L = \frac{1}{2} |b'_2|^2 - \frac{1}{2} |a'_2|^2 = \frac{1}{2} |b'_2|^2 = |S'_{21}|^2 \frac{1}{2} |a'_1|^2 = |S'_{21}|^2 P_{\text{avg}} \quad (12.7.19)$$

It follows that the transducer and operating power gains are:

$$G_T = \frac{P_L}{P_{\text{avg}}} = |S'_{21}|^2, \quad G_p = \frac{P_L}{P_{\text{in}}} = \frac{|S'_{21}|^2}{1 - |S'_{11}|^2} \quad (12.7.20)$$

These also follow from the explicit expressions (12.7.13) and Eqs. (12.6.10) and (12.6.11). We can also express the available power gain in terms of the generalized S-parameters, that is,  $G_a = |S'_{21}|^2 / (1 - |S'_{22}|^2)$ . Thus, we summarize:

$$G_T = |S'_{21}|^2, \quad G_a = \frac{|S'_{21}|^2}{1 - |S'_{22}|^2}, \quad G_p = \frac{|S'_{21}|^2}{1 - |S'_{11}|^2} \tag{12.7.21}$$

When the load and generator are matched to the network, that is,  $\Gamma_{in} = \Gamma_G^*$  and  $\Gamma_L = \Gamma_{out}^*$ , the generalized reflections coefficients vanish,  $S'_{11} = S'_{22} = 0$ , making all the gains equal to each other.

### 12.8 Simultaneous Conjugate Matching

We saw that the transducer, available, and operating power gains become equal to the maximum available gain  $G_{MAG}$  when both the generator and the load are conjugately matched to the two-port, that is,  $\Gamma_{in} = \Gamma_G^*$  and  $\Gamma_L = \Gamma_{out}^*$ . Using Eq. (12.5.8), these conditions read explicitly:

$$\begin{aligned} \Gamma_G^* &= S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} = \frac{S_{11} - \Delta\Gamma_L}{1 - S_{22}\Gamma_L} \\ \Gamma_L^* &= S_{22} + \frac{S_{12}S_{21}\Gamma_G}{1 - S_{22}\Gamma_G} = \frac{S_{22} - \Delta\Gamma_G}{1 - S_{11}\Gamma_G} \end{aligned} \tag{12.8.1}$$

Assuming a bilateral two-port, Eqs. (12.8.1) can be solved in the two unknowns  $\Gamma_G, \Gamma_L$  (eliminating one of the unknowns gives a quadratic equation for the other.) The resulting solutions can be expressed in terms of the parameters (12.5.1):

$$\begin{aligned} \Gamma_G &= \frac{B_1 \mp \sqrt{B_1^2 - 4|C_1|^2}}{2C_1} \\ \Gamma_L &= \frac{B_2 \mp \sqrt{B_2^2 - 4|C_2|^2}}{2C_2} \end{aligned} \tag{12.8.2}$$

(simultaneous conjugate match)

where the minus signs are used when  $B_1 > 0$  and  $B_2 > 0$ , and the plus signs, otherwise. A necessary and sufficient condition for these solutions to have magnitudes  $|\Gamma_G| < 1$  and  $|\Gamma_L| < 1$  is that the Rollett stability factor be greater than unity,  $K > 1$ . This is satisfied when the two-port is unconditionally stable, which implies that  $K > 1$  and  $B_1 > 0, B_2 > 0$ .

A conjugate match exists also when the two-port is potentially unstable, but with  $K > 1$ . Necessarily, this means that  $B_1 < 0, B_2 < 0$ , and also  $|\Delta| > 1$ . Such cases are rare in practice. For example, most microwave transistors have either  $K > 1$  and are stable, or, they are potentially unstable with  $K < 1$  and  $|\Delta| < 1$ .

If the two-port is unilateral,  $S_{12} = 0$ , then the two equations (12.8.1) decouple, so that the optimum conjugately matched terminations are:

$$\Gamma_G = S_{11}^*, \quad \Gamma_L = S_{22}^* \tag{12.8.3}$$

(unilateral conjugate match)

The MATLAB function `smatch` implements Eqs. (12.8.2). It works only if  $K > 1$ . Its usage is as follows:

[gG, gL] = smatch(S);

% conjugate matched terminations  $\Gamma_{bG}, \Gamma_{bL}$

To realize such optimum conjugately matched terminations, matching networks must be used at the input and output of the two-port as shown in Fig. 12.8.1.

The input matching network can be thought as being effectively connected to the impedance  $Z_{in} = Z_G^*$  at its output terminals. It must transform  $Z_{in}$  into the actual impedance of the connected generator, typically,  $Z_0 = 50$  ohm.

The output matching network must transform the actual load impedance, here  $Z_0$ , into the optimum load impedance  $Z_L = Z_{out}^*$ .

 


Fig. 12.8.1 Input and output matching networks.

The matching networks may be realized in several possible ways, as discussed in Chap. 11. Stub matching, quarter-wavelength matching, or lumped  $L$ -section or  $\Pi$ -section networks may be used. In designing the matching networks, it proves convenient to first design the reverse network as mentioned in Sec. 1.1.13.

Fig. 12.8.2 shows the procedure for designing the output matching network using a reversed stub matching transformer or a reversed quarter-wave transformer with a parallel stub. In both cases the reversed network is designed to transform the load impedance  $Z_L^*$  into  $Z_0$ .

 


Fig. 12.8.2 Two types of output matching networks and their reversed networks..

**Example 12.8.1:** A microwave transistor amplifier uses the Hewlett-Packard AT-41410 NPN bipolar transistor having  $S$ -parameters at 2 GHz [854]:

$$S_{11} = 0.61 \angle -165^\circ, \quad S_{21} = 3.72 \angle 59^\circ, \quad S_{12} = 0.05 \angle 42^\circ, \quad S_{22} = 0.45 \angle -48^\circ$$

Determine the optimum conjugately matched source and load terminations, and design appropriate input and output matching networks.

**Solution:** This is the continuation of Example 12.6.1. The transistor is stable with  $K = 1.1752$  and  $|\Delta| = 0.1086$ . The function `smatch` gives:

$$[ \Gamma_G, \Gamma_L ] = \text{smatch}(S) \Rightarrow \Gamma_G = 0.8179 \angle -162.6697^\circ, \quad \Gamma_L = 0.7495 \angle 52.5658^\circ$$

The corresponding source, load, input, and output impedances are (with  $Z_0 = 50$ ):

$$Z_G = Z_{in}^* = 5.1241 - 7.5417j \Omega, \quad Z_L = Z_{out}^* = 33.6758 + 91.4816j \Omega$$

The locations of the optimum reflection coefficients on the Smith chart are shown in Fig. 12.8.3. For comparison, the unilateral solutions of Eq. (12.8.3) are also shown.

 


Fig. 12.8.3 Optimum load and source reflection coefficients.

We consider three types of matching networks: (a) microstrip single-stub matching networks with open shunt stubs, shown in Fig. 12.8.4, (b) microstrip quarter-wavelength matching networks with open  $\lambda/8$  or  $3\lambda/8$  stubs, shown in Fig. 12.8.5, and (c)  $L$ -section matching networks, shown in 12.8.6.

 


Fig. 12.8.4 Input and output stub matching networks.

In Fig. 12.8.4, the input stub must transform  $Z_{in}$  to  $Z_0$ . It can be designed with the help of the function `stub1`, which gives the two solutions:

$$d1 = \text{stub1}(Z_{in}/Z_0, 'po') = \begin{bmatrix} 0.3038 & 0.4271 \\ 0.1962 & 0.0247 \end{bmatrix}$$

We choose the lower one, which has the shortest lengths. Thus, the stub length is  $d = 0.1962\lambda$  and the segment length  $l = 0.0247\lambda$ . Both segments can be realized with microstrips of characteristic impedance  $Z_0 = 50$  ohm. Similarly, the output matching network can be designed by:

$$d1 = \text{stub1}(Z_{out}/Z_0, 'po') = \begin{bmatrix} 0.3162 & 0.1194 \\ 0.1838 & 0.2346 \end{bmatrix}$$

Again, we choose the lower solutions,  $d = 0.1838\lambda$  and  $l = 0.2346\lambda$ . The solutions using shorted shunt stubs are:

$$\text{stub1}(Z_{in}/Z_0) = \begin{bmatrix} 0.0538 & 0.4271 \\ 0.4462 & 0.0247 \end{bmatrix}, \quad \text{stub1}(Z_{out}/Z_0) = \begin{bmatrix} 0.0662 & 0.1194 \\ 0.4338 & 0.2346 \end{bmatrix}$$

Using microstrip lines with alumina substrate ( $\epsilon_r = 9.8$ ), we obtain the following values for the width-to-height ratio, effective permittivity, and wavelength:

$$\begin{aligned} u &= \frac{w}{h} = \text{mstrip}(\epsilon_r, Z_0) = 0.9711 \\ \epsilon_{\text{eff}} &= \text{mstripa}(\epsilon_r, u) = 6.5630 \\ \lambda &= \frac{\lambda_0}{\sqrt{\epsilon_{\text{eff}}}} = 5.8552 \text{ cm} \end{aligned}$$

where  $\lambda_0 = 1.5$  cm is the free-space wavelength at 2 GHz. It follows that the actual segment lengths are  $d = 1.1486$  cm,  $l = 0.1447$  cm for the input network, and  $d = 1.0763$  cm,  $l = 1.3734$  cm for the output network.

In the quarter-wavelength method shown in Fig. 12.8.5, we use the function `qwt2` to carry out the design of the required impedances of the microstrip segments. We have for the input and output networks:

$$\begin{aligned} [Z_1, Z_2] &= \text{qwt2}(Z_{in}, Z_0) = [28.4817, -11.0232] \Omega \\ [Z_1, Z_2] &= \text{qwt2}(Z_{out}, Z_0) = [118.7832, 103.8782] \Omega \end{aligned}$$

For the input case, we find  $Z_2 = -11.0232 \Omega$ , which means that we should use either a  $3\lambda/8$ -shorted stub or a  $\lambda/8$ -opened one. We choose the latter. Similarly, for the output case, we have  $Z_2 = 103.8782 \Omega$ , and we choose a  $3\lambda/8$ -opened stub. The parameters of each microstrip segment are:

$$\begin{aligned} Z_1 &= 28.4817 \Omega, & u &= 2.5832, & \epsilon_{\text{eff}} &= 7.2325, & \lambda &= 5.578 \text{ cm}, & \lambda/4 &= 1.394 \text{ cm} \\ Z_2 &= 11.0232 \Omega, & u &= 8.9424, & \epsilon_{\text{eff}} &= 8.2974, & \lambda &= 5.207 \text{ cm}, & \lambda/8 &= 0.651 \text{ cm} \\ Z_1 &= 118.7832 \Omega, & u &= 0.0656, & \epsilon_{\text{eff}} &= 5.8790, & \lambda &= 6.186 \text{ cm}, & \lambda/4 &= 1.547 \text{ cm} \\ Z_2 &= 103.8782 \Omega, & u &= 0.1169, & \epsilon_{\text{eff}} &= 7.9503, & \lambda &= 6.149 \text{ cm}, & 3\lambda/8 &= 2.306 \text{ cm} \end{aligned}$$

Finally, the designs using  $L$ -sections shown in Fig. 12.8.6, can be carried out with the help of the function `lmatch`. We have the dual solutions for the input and output networks:

 


Fig. 12.8.5 Quarter-wavelength matching networks with  $\lambda/8$ -stubs.

 


Fig. 12.8.6 Input and output matching with L-sections.

$$[X_1, X_2] = \text{lmatch}(Z_0, Z_{in}, 'n') = \begin{bmatrix} 16.8955 & -22.7058 \\ -16.8955 & 7.6223 \end{bmatrix}$$

$$[X_1, X_2] = \text{lmatch}(Z_{out}, Z_0, 'n') = \begin{bmatrix} 57.9268 & -107.7472 \\ 502.4796 & 7.6223 \end{bmatrix}$$

According to the usage of `lmatch`, the output network transforms  $Z_0$  into  $Z_{out}^*$ , but that is equal to  $Z_L$  as required.

Choosing the first rows as the solutions in both cases, the shunt part  $X_1$  will be inductive and the series part  $X_2$ , capacitive. At 2 GHz, we find the element values:

$$L_1 = \frac{X_1}{\omega} = 1.3445 \text{ nH}, \quad C_1 = -\frac{1}{\omega X_2} = 3.5047 \text{ pF}$$

$$L_2 = \frac{X_1}{\omega} = 4.6097 \text{ nH}, \quad C_2 = -\frac{1}{\omega X_2} = 0.7386 \text{ pF}$$

The output network, but not the input one, also admits a reversed L-section solution:

$$[X_1, X_2] = \text{lmatch}(Z_{out}, Z_0, 'r') = \begin{bmatrix} 71.8148 & 68.0353 \\ -71.8148 & 114.9280 \end{bmatrix}$$

The essential MATLAB code used to generate the above results was as follows:

```
Z0 = 50; f = 2; w=2*pi*f; lA0 = 30/f; er = 9.8; % f in GHz
S = smat([0.61 165 3.72 59 0.05 42 0.45 -48]); % S-matrix
[gG, gL] = smatch(S); % simultaneous conjugate match
```

```
smith; % draw Fig. 12.8.3
plot(gG, 'o'); plot(conj(S(1,1)), 'o');
plot(gL, 'o'); plot(conj(S(2,2)), 'o');
ZG = gZz(gG,Z0); Zin = conj(ZG);
ZL = gZz(gL,Z0); Zout = conj(ZL);

d1 = stub1(Zin/Z0, 'po'); % single-stub design
d1 = stub1(Zout/Z0, 'po');

u = mstrip(er,Z0); % microstrip w/h ratio
eff = mstripa(er,u); % effective permittivity
lA = lA0/sqrt(eff); % wavelength within microstrip

[Z1,Z2] = qwt2(Zin, Z0); % quarter-wavelength with λ/8 stub
[Z1,Z2] = qwt2(Zout, Z0);

X12 = lmatch(Z0,Zin,'n'); L1 = X12(1,1)/w; C1 = -1/(w * X12(1,2))*1e3;
X12 = lmatch(Zout,Z0,'n'); L2 = X12(1,1)/w; C2 = -1/(w * X12(1,2))*1e3;
X12 = lmatch(Zout,Z0,'r'); % L, C in units of nH and pF
```

One could replace the stubs with balanced stubs, as discussed in Sec. 11.9, or use  $\Pi$ - or  $T$ -sections instead of L-sections. □

### 12.9 Power Gain Circles

For a stable two-port, the maximum transducer gain is achieved at single pair of points  $\Gamma_G, \Gamma_L$ . When the gain  $G$  is required to be less than  $G_{MAG}$ , there will be many possible pairs  $\Gamma_G, \Gamma_L$  at which the gain  $G$  is realized. The locus of such points  $\Gamma_G$  and  $\Gamma_L$  on the  $\Gamma$ -plane is typically a circle of the form:

$$|\Gamma - c| = r \quad (12.9.1)$$

where  $c, r$  are the center and radius of the circle and depend on the desired value of the gain  $G$ .

In practice, several types of such circles are used, such as unilateral, operating, and available power gain circles, as well as constant noise figure circles, constant SWR circles, and others.

The gain circles allow one to select appropriate values for  $\Gamma_G, \Gamma_L$  that, in addition to providing the desired gain, also satisfy other requirements, such as striking a balance between minimizing the noise figure and maximizing the gain.

The MATLAB function `sgcirc` calculates the stability circles as well as the operating, available, and unilateral gain circles. Its complete usage is:

```
[c,r] = sgcirc(S, 's'); % source stability circle
[c,r] = sgcirc(S, 'l'); % load stability circle
[c,r] = sgcirc(S, 'p',G); % operating power gain circle
[c,r] = sgcirc(S, 'a',G); % available power gain circle
[c,r] = sgcirc(S, 'ui',G); % unilateral input gain circle
[c,r] = sgcirc(S, 'uo',G); % unilateral output gain circle
```



where in the last four cases  $G$  is the desired gain in dB.

## 12.10 Unilateral Gain Circles

We consider only the unconditionally stable unilateral case, which has  $|S_{11}| < 1$  and  $|S_{22}| < 1$ . The dependence of the transducer power gain on  $\Gamma_G$  and  $\Gamma_L$  decouples and the value of the gain may be adjusted by separately choosing  $\Gamma_G$  and  $\Gamma_L$ . We have from Eq. (12.6.14):

$$G_T = \frac{1 - |\Gamma_G|^2}{|1 - S_{11}\Gamma_G|^2} \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2} = G_G |S_{21}|^2 G_L \quad (12.10.1)$$

The input and output gain factors  $G_G, G_L$  satisfy the inequalities (12.6.24). Concentrating on the output gain factor, the corresponding gain circle is obtained as the locus of points  $\Gamma_L$  that will lead to a fixed value, say  $G_L = G$ , which necessarily must be less than the maximum  $G_2$  given in Eq. (12.6.23), that is,

$$\frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2} = G \leq G_2 = \frac{1}{1 - |S_{22}|^2} \quad (12.10.2)$$

Normalizing the gain  $G$  to its maximum value  $g = G/G_2 = G(1 - |S_{22}|^2)$ , we may rewrite (12.10.2) in the form:

$$\frac{(1 - |\Gamma_L|^2)(1 - |S_{22}|^2)}{|1 - S_{22}\Gamma_L|^2} = g \leq 1 \quad (12.10.3)$$

This equation can easily be rearranged into the equation of a circle  $|\Gamma_L - c| = r$ , with center and radius given by:

$$c = \frac{gS_{22}^*}{1 - (1 - g)|S_{22}|^2}, \quad r = \frac{\sqrt{1 - g}(1 - |S_{22}|^2)}{1 - (1 - g)|S_{22}|^2} \quad (12.10.4)$$

When  $g = 1$  or  $G = G_2$ , the gain circle collapses onto a single point, that is, the optimum point  $\Gamma_L = S_{22}^*$ . Similarly, we find for the constant gain circles of the input gain factor:

$$c = \frac{gS_{11}^*}{1 - (1 - g)|S_{11}|^2}, \quad r = \frac{\sqrt{1 - g}(1 - |S_{11}|^2)}{1 - (1 - g)|S_{11}|^2} \quad (12.10.5)$$

where here,  $g = G/G_1 = G(1 - |S_{11}|^2)$  and the circles are  $|\Gamma_G - c| = r$ .

Both sets of  $c, r$  satisfy the conditions  $|c| < 1$  and  $|c| + r < 1$ , the latter implying that the circles lie entirely within the unit circle  $|\Gamma| < 1$ , that is, within the Smith chart.

**Example 12.10.1:** A unilateral microwave transistor has  $S$ -parameters:

$$S_{11} = 0.8 \angle 120^\circ, \quad S_{21} = 4 \angle 60^\circ, \quad S_{12} = 0, \quad S_{22} = 0.2 \angle -30^\circ$$

The unilateral MAG and the maximum input and output gains are obtained as follows:

$$G_{\text{MAG},u} = \text{sgain}(S, 'u') = 16.66 \text{ dB}$$

$$G_1 = \text{sgain}(S, 'u1') = 4.44 \text{ dB}$$

$$G_2 = \text{sgain}(S, 'uo') = 0.18 \text{ dB}$$

Most of the gain is accounted for by the factor  $|S_{21}|^2$ , which is 12.04 dB. The constant input gain circles for  $G_G = 1, 2, 3$  dB are shown in Fig. 12.10.1. Their centers lie along the ray to  $S_{11}^*$ . For example, the center and radius of the 3-dB case were computed by

$$[c_3, r_3] = \text{sgcirc}(S, 'u1', 3) \Rightarrow c_3 = 0.701 \angle -120^\circ, \quad r_3 = 0.233$$

 


Fig. 12.10.1 Unilateral input gain circles.

Because the output does not provide much gain, we may choose the optimum value  $\Gamma_L = S_{22}^* = 0.2 \angle 30^\circ$ . Then, with any point  $\Gamma_G$  along the 3-dB input gain circle the total transducer gain will be in dB:

$$G_T = G_G + |S_{21}|^2 + G_L = 3 + 12.04 + 0.18 = 15.22 \text{ dB}$$

Points along the 3-dB circle are parametrized as  $\Gamma_G = c_3 + r_3 e^{j\phi}$ , where  $\phi$  is any angle. Choosing  $\phi = \arg(S_{11}^*) - \pi$  will correspond to the point on the circle that lies closest to the origin, that is,  $\Gamma_G = 0.468 \angle -120^\circ$ , as shown in Fig. 12.10.1. The corresponding generator and load impedances will be:

$$Z_G = 69.21 + 14.42j \Omega, \quad Z_L = 23.15 - 24.02j \Omega$$

The MATLAB code used to generate these circles was:

```
S = smat([0.8, 120, 4, 60, 0, 0, 0.2, -30]);
[c1, r1] = sgcirc(S, 'u1', 1);
[c2, r2] = sgcirc(S, 'u1', 2);
[c3, r3] = sgcirc(S, 'u1', 3);
smith; smithcir(c1, r1); smithcir(c2, r2); smithcir(c3, r3);
c = exp(-j*angle(S(1,1))); line([0, real(c)], [0, imag(c)]);
gG = c3 - r3*exp(j*angle(c3));
plot(conj(S(1,1)), '.'); plot(conj(S(2,2)), '.'); plot(gG, '.');
```

The input and output matching networks can be designed using open shunt stubs as in Fig. 12.8.4. The stub lengths are found to be (with  $Z_0 = 50 \Omega$ ):

$$dl = \text{stub1}(Z_G^*/Z_0, 'po') = \begin{bmatrix} 0.3704 & 0.3304 \\ 0.1296 & 0.0029 \end{bmatrix}$$

$$dl = \text{stub1}(Z_L^*/Z_0, 'po') = \begin{bmatrix} 0.4383 & 0.0994 \\ 0.0617 & 0.3173 \end{bmatrix}$$

Choosing the shortest lengths, we have for the input network  $d = 0.1296\lambda$ ,  $l = 0.0029\lambda$ , and for the output network,  $d = 0.0617\lambda$ ,  $l = 0.3173\lambda$ . Fig. 12.10.2 depicts the complete matching circuit.  $\square$

 


Fig. 12.10.2 Input and output stub matching networks.

### 12.11 Operating and Available Power Gain Circles

Because the transducer power gain  $G_T$  depends on two independent parameters—the source and load reflection coefficients—it is difficult to find the simultaneous locus of points for  $I_G, I_L$  that will result in a given value for the gain.

If the generator is matched,  $I_{in} = I_G^*$ , then the transducer gain becomes equal to the operating gain  $G_T = G_p$  and depends only on the load reflection coefficient  $I_L$ . The locus of points  $I_L$  that result in fixed values of  $G_p$  are the *operating power gain circles*. Similarly, the *available power gain circles* are obtained by matching the load end,  $I_L = I_{out}^*$ , and varying  $I_G$  to achieve fixed values of the available power gain.

Using Eqs. (12.6.11) and (12.5.8), the conditions for achieving a constant value, say  $G$ , for the operating or the available power gains are:

$$G_p = \frac{1}{1 - |I_{in}|^2} \frac{|S_{21}|^2}{|1 - S_{22}I_L|^2} \frac{1 - |I_L|^2}{1 - S_{22}I_L} = G, \quad I_G^* = I_{in} = \frac{S_{11} - \Delta I_L}{1 - S_{22}I_L}$$

$$G_a = \frac{1 - |I_G|^2}{|1 - S_{11}I_G|^2} \frac{|S_{21}|^2}{1 - |I_{out}|^2} = G, \quad I_L^* = I_{out} = \frac{S_{22} - \Delta I_G}{1 - S_{11}I_G}$$

We consider the operating gain first. Defining the normalized gain  $g = G/|S_{21}|^2$ , substituting  $I_{in}$ , and using the definitions (12.5.1), we obtain the condition:

$$g = \frac{1 - |I_L|^2}{|1 - S_{22}I_L|^2 - |S_{11} - \Delta I_L|^2}$$

$$= \frac{1 - |I_L|^2}{(|S_{22}|^2 - |\Delta|^2)|I_L|^2 - (S_{22} - \Delta S_{11}^*)I_L - (S_{22}^* - \Delta^* S_{11})I_L^* + 1 - |S_{11}|^2}$$

$$= \frac{D_2 |I_L|^2 - C_2 I_L - C_2^* I_L^* + 1 - |S_{11}|^2}{1 - |I_L|^2}$$

This can be rearranged into the form:

$$|I_L|^2 - \frac{gC_2}{1 + gD_2} I_L - \frac{gC_2^*}{1 + gD_2} I_L^* = \frac{1 - g(1 - |S_{11}|^2)}{1 + gD_2}$$

and then into the circle form:

$$\left| I_L - \frac{gC_2^*}{1 + gD_2} \right|^2 = \frac{g^2 |C_2|^2}{(1 + gD_2)^2} + \frac{1 - g(1 - |S_{11}|^2)}{1 + gD_2}$$

Using the identities (12.5.2) and  $1 - |S_{11}|^2 = 2K|S_{12}S_{21}| + D_2$ , which follows from (12.5.1), the right-hand side of the above circle form can be written as:

$$\frac{g^2 |C_2|^2}{(1 + gD_2)^2} + \frac{1 - g(1 - |S_{11}|^2)}{1 + gD_2} = \frac{g^2 |S_{12}S_{21}|^2 - 2gK|S_{12}S_{21}| + 1}{(1 + gD_2)^2} \quad (12.11.2)$$

Thus, the *operating power gain circle* will be  $|I_L - c|^2 = r^2$  with center and radius:

$$c = \frac{gC_2^*}{1 + gD_2}, \quad r = \frac{\sqrt{g^2 |S_{12}S_{21}|^2 - 2gK|S_{12}S_{21}| + 1}}{|1 + gD_2|} \quad (12.11.3)$$

The points  $I_L$  on this circle result into the value  $G_p = G$  for the operating gain. Such points can be parametrized as  $I_L = c + re^{j\phi}$ , where  $0 \leq \phi \leq 2\pi$ . As  $I_L$  traces this circle, the conjugately matched source coefficient  $I_G = I_{in}^*$  will also trace a circle because  $I_{in}$  is related to  $I_L$  by the bilinear transformation (12.5.8).

In a similar fashion, we find the *available power gain circles* to be  $|I_G - c|^2 = r^2$ , where  $g = G/|S_{21}|^2$  and:

$$c = \frac{gC_1^*}{1 + gD_1}, \quad r = \frac{\sqrt{g^2 |S_{12}S_{21}|^2 - 2gK|S_{12}S_{21}| + 1}}{|1 + gD_1|} \quad (12.11.4)$$

We recall from Sec. 12.5 that the centers of the load and source stability circles were  $c_L = C_2^*/D_2$  and  $c_G = C_1^*/D_1$ . It follows that the centers of the operating power gain circles are along the same ray as  $c_L$ , and the centers of the available gain circles are along the same ray as  $c_G$ .

For an unconditionally stable two-port, the gain  $G$  must be  $0 \leq G \leq G_{MAG}$ , with  $G_{MAG}$  given by Eq. (12.6.20). It can be shown easily that the quantities under the square

roots in the definitions of the radii  $r$  in Eqs. (12.1.1.3) and (12.1.1.4) are non-negative. The gain circles lie inside the unit circle for all such values of  $G$ . The radii  $r$  vanish when  $G = G_{\text{MAG}}$ , that is, the circles collapse into single points corresponding to the simultaneous conjugate matched solutions of Eq. (12.8.2).

The MATLAB function `sgcirc` calculates the center and radii  $c, r$  of the operating and available power gain circles. It has usage, where  $G$  must be entered in dB:

```
[c,r] = sgcirc(S,'p',G);      % operating power gain circle
[c,r] = sgcirc(S,'a',G);    % available power gain circle
```

**Example 12.11.1:** A microwave transistor amplifier uses the Hewlett-Packard AT-41410 NPN bipolar transistor with the following  $S$ -parameters at 2 GHz [854]:

$$S_{11} = 0.61 \angle 165^\circ, \quad S_{21} = 3.72 \angle 59^\circ, \quad S_{12} = 0.05 \angle 42^\circ, \quad S_{22} = 0.45 \angle -48^\circ$$

Calculate  $G_{\text{MAG}}$  and plot the operating and available power gain circles for  $G = 13, 14, 15$  dB. Then, design source and load matching circuits for the case  $G = 15$  dB by choosing the reflection coefficient that has the smallest magnitude.

**Solution:** The MAG was calculated in Example 12.6.1,  $G_{\text{MAG}} = 16.18$  dB. The gain circles and the corresponding load and source stability circles are shown in Fig. 12.11.1. The operating gain and load stability circles were computed and plotted by the MATLAB statements:

```
[c1,r1] = sgcirc(S,'p',13);    % cb1 = 0.4443 ∠ 52.56°, rb1 = 0.5212
[c2,r2] = sgcirc(S,'p',14);    % cb2 = 0.5297 ∠ 52.56°, rb2 = 0.4205
[c3,r3] = sgcirc(S,'p',15);    % cb3 = 0.6253 ∠ 52.56°, rb3 = 0.2968
[cL,rL] = sgcirc(S,'l');       % cbL = 2.0600 ∠ 52.56°, rbL = 0.9753

smith; smithcir(cL,rL,1.7);    % display portion of circle with |ΓBL| ≤ 1.7
smithcir(c1,r1); smithcir(c2,r2); smithcir(c3,r3);
```

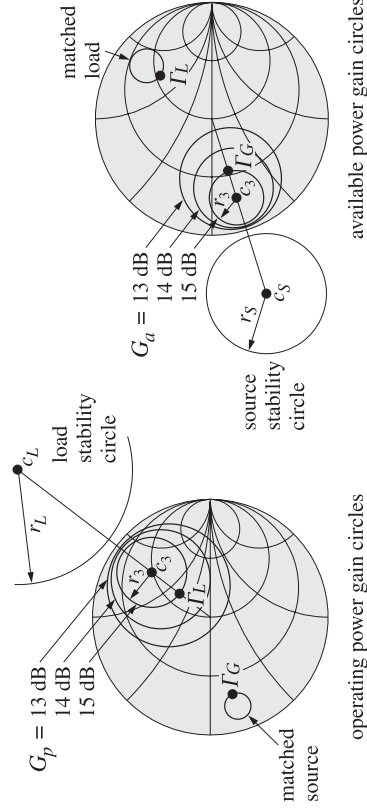


Fig. 12.11.1 Operating and available power gain circles.

The gain circles lie entirely within the unit circle, for example, we have  $r_3 + |c_3| = 0.9221 < 1$ , and their centers lie along the ray of  $c_L$ . As  $\Gamma_L$  traces the 15-dB circle, the corresponding  $\Gamma_G = \Gamma_{\text{in}}^*$  traces its own circle, also lying within the unit circle. The following MATLAB code computes and adds that circle to the above Smith chart plots:

```
phi = linspace(0,2*pi,361);    % equally spaced angles at 1° intervals
gammaL = c3 + r3 * exp(j*phi); % points on 15-dB operating gain circle
gammaG = conj(gin(S,gammaL)); % circle of conjugate matched source points
plot(gammaG);
```

In particular, the point  $\Gamma_L$  on the 15-dB circle that lies closest to the origin is  $\Gamma_L = c_3 - r_3 e^{j \text{ang} c_3} = 0.3285 \angle 52.56^\circ$ . The corresponding matched load will be  $\Gamma_G = \Gamma_{\text{in}}^* = 0.6805 \angle -163.88^\circ$ . These and the corresponding source and load impedances were computed by the MATLAB statements:

```
gL = c3 - r3*exp(j*ang(c3));    % zL = gZz(gL);
gG = conj(gin(S,gL));          % zG = gZz(gG);
```

The source and load impedances normalized to  $Z_0 = 50$  ohm are:

$$Z_G = \frac{Z_G}{Z_0} = 0.1938 - 0.1363j, \quad Z_L = \frac{Z_L}{Z_0} = 1.2590 + 0.7361j$$

The matching circuits can be designed in a variety of ways as in Example 12.8.1. Using open shunt stubs, we can determine the stub and line segment lengths with the help of the function `stubl`:

```
d1 = stubl(zG*, 'po') = [ 0.3286  0.4122
                        0.1714  0.0431 ]
d1 = stubl(zL*, 'po') = [ 0.4033  0.0786
                        0.0967  0.2754 ]
```

In both cases, we may choose the lower solutions as they have shorter total length  $d + l$ . The available power gain circles can be determined in a similar fashion with the help of the MATLAB statements:

```
[c1,r1] = sgcirc(S,'a',13);    % cb1 = 0.5384 ∠ -162.67°, rb1 = 0.4373
[c2,r2] = sgcirc(S,'a',14);    % cb2 = 0.6227 ∠ -162.67°, rb2 = 0.3422
[c3,r3] = sgcirc(S,'a',15);    % cb3 = 0.7111 ∠ -162.67°, rb3 = 0.2337
[cG,rG] = sgcirc(S,'s');       % cbG = 1.5748 ∠ -162.67°, rbG = 0.5162

smith; smithcir(cG,rG);       % plot entire source stability circle
smithcir(c1,r1); smithcir(c2,r2); smithcir(c3,r3);
```

Again, the circles lie entirely within the unit circle. As  $\Gamma_G$  traces the 15-dB circle, the corresponding matched load  $\Gamma_L = \Gamma_{\text{out}}^*$  traces its own circle on the  $\Gamma$ -plane. It can be plotted with:

```
phi = linspace(0,2*pi,361);    % equally spaced angles at 1° intervals
gammaG = c3 + r3 * exp(j*phi); % points on 15-dB available gain circle
gammaL = conj(gout(S,gammaG)); % circle of conjugate matched loads
plot(gammaL);
```

In particular, the point  $I_G = c_3 - r_3 e^{j \arg c_3} = 0.4774 \angle -162.67^\circ$  lies closest to the origin. The corresponding matched load will have  $I_L = I_{\text{out}}^* = 0.5728 \angle 50.76^\circ$ . The resulting normalized impedances are:

$$z_G = \frac{Z_G}{Z_0} = 0.3609 - 0.1329j, \quad z_L = \frac{Z_L}{Z_0} = 1.1135 + 1.4704j$$

and the corresponding stub matching networks will have lengths:

$$\text{stub1}(z_G^*, 'po') = \begin{bmatrix} 0.3684 & 0.3905 & 0.3488 & 0.1030 \\ 0.1316 & 0.0613 & 0.1512 & 0.2560 \end{bmatrix}, \quad \text{stub1}(z_L^*, 'po') = \begin{bmatrix} 0.3488 & 0.1030 \\ 0.1512 & 0.2560 \end{bmatrix}$$

The lower solutions have the shortest lengths. For both the operating and available gain cases, the stub matching circuits will be similar to those in Fig. 12.8.4.  $\square$

When the two-port is potentially unstable (but with  $|S_{11}| < 1$  and  $|S_{22}| < 1$ ), the stability circles intersect with the unit-circle, as shown in Fig. 12.5.2. In this case, the operating and available power gain circles also intersect the unit-circle and at the *same* points as the stability circles.

We demonstrate this in the specific case of  $K < 1$ ,  $|S_{11}| < 1$ ,  $|S_{22}| < 1$ , but with  $D_2 > 0$ , an example of which is shown in Fig. 12.11.2. The intersection of an operating gain circle with the unit-circle is obtained by setting  $|I_L| = 1$  in the circle equation  $|I_L - c| = r$ . Writing  $I_L = e^{j\theta_L}$  and  $c = |c|e^{j\theta_c}$ , we have:

$$r^2 = |I_L - c|^2 = 1 - 2|c| \cos(\theta_L - \theta_c) + |c|^2 \Rightarrow \cos(\theta_L - \theta_c) = \frac{1 + |c|^2 - r^2}{2|c|}$$

Similarly, the intersection of the load stability circle with the unit-circle leads to the relationship:

$$r_L^2 = |I_L - c_L|^2 = 1 - 2|c_L| \cos(\theta_L - \theta_{c_L}) + |c_L|^2 \Rightarrow \cos(\theta_L - \theta_{c_L}) = \frac{1 + |c_L|^2 - r_L^2}{2|c_L|}$$

Because  $c = gC_2^*/(1 + gD_2)$ ,  $c_L = C_2^*/D_2$ , and  $D_2 > 0$ , it follows that the phase angles of  $c$  and  $c_L$  will be equal,  $\theta_c = \theta_{c_L}$ . Therefore, in order for the load stability circle and the gain circle to intersect the unit-circle at the same  $I_L = e^{j\theta_L}$ , the following condition must be satisfied:

$$\cos(\theta_L - \theta_c) = \frac{1 + |c|^2 - r^2}{2|c|} = \frac{1 + |c_L|^2 - r_L^2}{2|c_L|} \quad (12.11.5)$$

Using the identities  $1 - |S_{11}|^2 = B_2 - D_2$  and  $1 - |S_{11}|^2 = (|c_L|^2 - r_L^2)/D_2$ , which follow from Eqs. (12.5.1) and (12.5.6), we obtain:

$$\frac{1 + |c_L|^2 - r_L^2}{2|c_L|} = \frac{1 + (B_2 - D_2)/D_2}{2|C_2|/|D_2|} = \frac{B_2}{2|C_2|}$$

where we used  $D_2 > 0$ . Similarly, Eq. (12.11.2) can be written in the form:

$$r^2 = |c|^2 + \frac{1 - g(1 - |S_{11}|^2)}{1 + gD_2} \Rightarrow |c|^2 - r^2 = \frac{g(1 - |S_{11}|^2) - 1}{1 + gD_2} = \frac{g(B_2 - D_2) - 1}{1 + gD_2}$$

Therefore, we have:

$$\frac{1 + |c|^2 - r^2}{2|c|} = \frac{1 + (g(B_2 - D_2) - 1)/(1 + gD_2)}{2|C_2|} = \frac{B_2}{2|C_2|}$$

Thus, Eq. (12.11.5) is satisfied. This condition has two solutions for  $\theta_L$  that correspond to the two points of intersection with the unit-circle. When  $D_2 > 0$ , we have  $\arg c = \arg C_2^* = -\arg C_2$ . Therefore, the two solutions for  $I_L = e^{j\theta_L}$  will be:

$$I_L = e^{j\theta_L}, \quad \theta_L = -\arg(C_2) \pm \arccos\left(\frac{B_2}{2|C_2|}\right) \quad (12.11.6)$$

Similarly, the points of intersection of the unit-circle and the available gain circles and source stability circle are:

$$I_G = e^{j\theta_G}, \quad \theta_G = -\arg(C_1) \pm \arccos\left(\frac{B_1}{2|C_1|}\right) \quad (12.11.7)$$

Actually, these expressions work also when  $D_2 < 0$  or  $D_1 < 0$ .

**Example 12.11.2:** The microwave transistor Hewlett-Packard AT-41410 NPN is potentially unstable at 1 GHz with the following  $S$ -parameters [854]:

$$S_{11} = 0.6 \angle -163^\circ, \quad S_{21} = 7.12 \angle 86^\circ, \quad S_{12} = 0.039 \angle 35^\circ, \quad S_{22} = 0.50 \angle -38^\circ$$

Calculate  $G_{\text{MSG}}$  and plot the operating and available power gain circles for  $G = 20, 21, 22$  dB. Then, design source and load matching circuits for the 22-dB case by choosing the reflection coefficients that have the smallest magnitudes.

**Solution:** The MSG computed from Eq. (12.6.2) is  $G_{\text{MSG}} = 22.61$  dB. Fig. 12.11.2 depicts the operating and available power gain circles as well as the load and source stability circles. The stability parameters are:  $K = 0.7667$ ,  $\mu_1 = 0.8643$ ,  $|\Delta| = 0.1893$ ,  $D_{b1} = 0.3242$ ,  $D_{b2} = 0.2142$ . The computations and plots are done with the following MATLAB code:<sup>†</sup>

```
S = smat([0.60, -163, 7.12, 86, 0.039, 35, 0.50, -38]); % S-parameters
[K,mu,D,B1,B2,C1,C2,D1,D2] = sparm(S); % stability parameters
Gmsg = db(ssgain(S,'msg')); % GMSG = 22.61 dB
% operating power gain circles:
[C1,r1] = sgcirc(S,'p',20); % cb1 = 0.6418 ∠ 50.80°, rb1 = 0.4768
[C2,r2] = sgcirc(S,'p',21); % cb2 = 0.7502 ∠ 50.80°, rb2 = 0.4221
[C3,r3] = sgcirc(S,'p',22); % cb3 = 0.8666 ∠ 50.80°, rb3 = 0.3893
% load and source stability circles:
[CL,rl] = sgcirc(S,'l'); % cbL = 2.1608 ∠ 50.80°, rBL = 1.2965
[CG,rg] = sgcirc(S,'s'); % cbG = 1.7456 ∠ 171.69°, rbG = 0.8566
smith; smithcir(CL,rl,1.5); smithcir(CG,rg,1.5); % plot Smith charts
smithcir(C1,r1); smithcir(C2,r2); smithcir(C3,r3); % plot gain circles
gl = c3 - r3*exp(j*angTe(c3)); % TBL of smallest magnitude
gg = conj(gin(S,gl)); % corresponding matched TbG
plot(gl,''); plot(rg,'');
% The function db converts absolute scales to dB. The function ab converts from dB to absolute units.
```

<sup>†</sup>The function db converts absolute scales to dB. The function ab converts from dB to absolute units.

 


Fig. 12.11.2 Operating and available power gain circles.

```
[c1,r1] = sgcirc(S,'a',20);
[c2,r2] = sgcirc(S,'a',21);
[c3,r3] = sgcirc(S,'a',22);

% available power gain circles:
% cb1 = 0.6809∠171.69°, rb1 = 0.4137
% cb2 = 0.7786∠171.69°, rb2 = 0.3582
% cb3 = 0.8787∠171.69°, rb3 = 0.3228

figure;
smith(cL,rL,1.5); smith(cG,rG,1.5);
smith(c1,r1); smith(c2,r2); smith(c3,r3);

gG = c3 - r3*exp(j*angle(c3));
gL = conj(gout(S,gG));
plot(gL, '.', 'b'); plot(gG, '.', 'r');
```

Because  $D_1 > 0$  and  $D_2 > 0$ , the stability regions are the portions of the unit-circle that lie outside the source and load stability circles. We note that the operating gain circles intersect the unit-circle at exactly the same points as the load stability circle, and the available gain circles intersect it at the same points as the source stability circle.

The value of  $\Gamma_L$  on the 22-dB operating gain circle that lies closest to the origin is  $\Gamma_L = c_3 - r_3 e^{j \arg c_3} = 0.4773 \angle 50.80^\circ$  and the corresponding matched source is  $\Gamma_G = \Gamma_{in}^* = 0.7632 \angle 167.69^\circ$ . We note that both  $\Gamma_L$  and  $\Gamma_G$  lie in their respective stability regions.

For the 22-dB available gain circle (also denoted by  $c_3, r_3$ ), the closest  $\Gamma_G$  to the origin will be  $\Gamma_G = c_3 - r_3 e^{j \arg c_3} = 0.5559 \angle 171.69^\circ$  with a corresponding matched load  $\Gamma_L = \Gamma_{out}^* = 0.7147 \angle 45.81^\circ$ . Again, both  $\Gamma_L, \Gamma_G$  lie in their stable regions.

Once the  $\Gamma_G, \Gamma_L$  have been determined, the corresponding matching input and output networks can be designed with the methods of Example 12.8.1.  $\square$

## 12.12 Noise Figure Circles

Every device is a source of internally generated noise. The noise entering the device and the internal noise must be added to obtain the total input system noise. If the device is an amplifier, the total system noise power will be amplified at the output by the gain of the device. If the output load is matched, this gain will be the available gain.

The internally generated noise is quantified in practice either by the *effective noise temperature*  $T_e$ , or by the *noise figure*  $F$  of the device. The internal noise power is given by  $P_n = kT_e B$ , where  $k$  is the Boltzmann constant and  $B$  the bandwidth in Hz. These concepts are discussed further in Sec. 14.8. The relationship between  $T_e$  and  $F$  is defined in terms of a standard reference temperature  $T_0 = 290$  K (degrees Kelvin):

$$F = 1 + \frac{T_e}{T_0} \tag{12.12.1}$$

The noise figure is usually quoted in dB,  $F_{dB} = 10 \log_{10} F$ . Because the available gain of a two-port depends on the source impedance  $Z_G$ , or the source reflection coefficient  $\Gamma_G$ , so will the noise figure.

The optimum source impedance  $Z_{Gopt}$  corresponds to the minimum noise figure  $F_{min}$  that can be achieved by the two-port. For other values of  $Z_G$ , the noise figure  $F$  is greater than  $F_{min}$  and is given by [97–100]:

$$F = F_{min} + \frac{R_n}{R_G |Z_{Gopt}|^2} |Z_G - Z_{Gopt}|^2 \tag{12.12.2}$$

where  $R_G = \text{Re}(Z_G)$  and  $R_n$  is an equivalent noise resistance. We note that  $F = F_{min}$  when  $Z_G = Z_{Gopt}$ . Defining the normalized noise resistance  $r_n = R_n/Z_0$ , where  $Z_0 = 50$  ohm, we may write Eq. (12.12.2) in terms of the corresponding source reflection coefficients:

$$F = F_{min} + 4r_n \frac{|I_G - I_{Gopt}|^2}{|1 + I_{Gopt}|^2 (1 - |I_G|^2)} \tag{12.12.3}$$

The parameters  $F_{min}, r_n$ , and  $I_{Gopt}$  characterize the noise properties of the two-port and are usually known.

In designing low-noise microwave amplifiers, one would want to achieve the minimum noise figure and the maximum gain. Unfortunately, the optimum source reflection coefficient  $I_{Gopt}$  does not necessarily correspond to the maximum available gain.

The noise figure circles and the available gain circles are useful tools that allow one to obtain a balance between low noise and high gain designs. The noise figure circles are the locus of points  $I_G$  that correspond to fixed values of  $F$ . They are obtained by rewriting Eq. (12.12.3) as the equation of a circle  $|I_G - c|^2 = r^2$ . We write Eq. (12.12.3) in the form:

$$\frac{|I_G - I_{Gopt}|^2}{1 - |I_G|^2} = N, \quad \text{where } N = \frac{(F - F_{min}) |1 + I_{Gopt}|^2}{4r_n} \tag{12.12.4}$$

which can be rearranged into the circle equation:

$$\left| I_G - \frac{\Gamma_{Gopt}}{N+1} \right|^2 = \frac{N^2 + N(1 - |I_{Gopt}|^2)}{(N+1)^2}$$

Thus, the center and radius of the noise figure circle are:

$$c = \frac{\Gamma_{Gopt}}{N+1}, \quad r = \frac{\sqrt{N^2 + N(1 - |I_{Gopt}|^2)}}{N+1} \tag{12.12.5}$$



The MATLAB function `nfcirc` implements Eq. (12.12.5). Its inputs are the noise parameters  $F_{\min}$ ,  $r_n$ ,  $I_{Gopt}$ , and the desired value of  $F$  in dB, and its outputs are  $c$ ,  $r$ :

```
[c,r] = nfcirc(F,Fmin,rn,gGopt); % noise figure circles
```

The function `nfig` implements Eq. (12.12.3). Its inputs are  $F_{\min}$ ,  $r_n$ ,  $I_{Gopt}$ , and a vector of values of  $I_G$ , and its output is the corresponding vector of values of  $F$ :

```
F = nfig(Fmin, rn, gGopt, gG); % calculate noise figure F in dB
```

**Example 12.12.1:** The microwave transistor of Example 12.11.1 has the following noise parameters at 2 GHz [854]:  $F_{\min} = 1.6$  dB,  $r_n = 0.16$ , and  $I_{Gopt} = 0.26 \angle 172^\circ$ .

Determine the matched load  $I_{Lopt}$  corresponding to  $I_{Gopt}$ , and calculate the available gain. Then, plot the noise figure circles for  $F = 1.7, 1.8, 1.9, 2.0$  dB.

For the 1.8-dB noise figure circle, determine  $I_G, I_L$  that correspond to the maximum possible available gain and design appropriate input and output matching networks.

**Solution:** The conjugate matched load corresponding to  $I_{Gopt}$  is:

$$I_{Lopt} = I_{out}^* = \left[ \frac{S_{22} - \Delta I_{Gopt}}{1 - S_{11} I_{Gopt}} \right]^* = 0.4927 \angle 52.50^\circ$$

The value of the available gain at  $I_{Gopt}$  is  $G_{a,opt} = 13.66$  dB. This is to be compared with the MAG of 16.18 dB determined in Example 12.11.1. To increase the available gain, we must also increase the noise figure. Fig. 12.12.1 shows the locations of the optimum reflection coefficients, as well as several noise figure circles.

The MATLAB code for generating this graph was:<sup>†</sup>

 


Fig. 12.12.1 Noise figure circles.

```
S = smat([0.61, 165, 3.72, 59, 0.05, 42, 0.45, -48]);
```

```
Fmin = 1.6; rn = 0.16; gGopt = p2c(0.26, 172);
```

<sup>†</sup>The function `p2c` converts from phasor form to cartesian complex form, and the function `c2p`, from cartesian to phasor form.

```
gMag = db(ssgain(S,'mag')); % maximum available gain
Gaopt = db(ssgain(S,gGopt,'a')); % available gain at I_bGopt

gLopt = conj(gout(S,gGopt)); % matched load

[c1,r1] = nfcirc(1.7,Fmin,rn,gGopt); % noise figure circles
[c2,r2] = nfcirc(1.8,Fmin,rn,gGopt);
[c3,r3] = nfcirc(1.9,Fmin,rn,gGopt);
[c4,r4] = nfcirc(2.0,Fmin,rn,gGopt);

smith; plot([gGopt, gLopt],'.');
smithcir(c1,r1); smithcir(c2,r2); smithcir(c3,r3); smithcir(c4,r4);
```

The larger the noise figure  $F$ , the larger the radius of its circle. As  $F$  increases, so does the available gain. But as the gain increases, the radius of its circle decreases. Thus, for a fixed value of  $F$ , there will be a maximum value of the available gain corresponding to that gain circle that has the smallest radius and is tangent to the noise figure circle.

In the extreme case of the maximum available gain, the available gain circle collapses to a point—the simultaneous conjugate matched point  $I_G = 0.8179 \angle -162.67^\circ$ —with a corresponding noise figure of  $F = 4.28$  dB. These results can be calculated by the MATLAB statements:

```
gG = smatch(S);
F = nfig(Fmin, rn, gopt, gG);
```

Thus, we see that increasing the gain comes at the price of increasing the noise figure. As  $I_G$  traces the  $F = 1.8$  dB circle, the available gain  $G_a$  varies as shown in Fig. 12.12.2. Points around this circle can be parametrized as  $I_G = C_2 + I_2 e^{j\phi}$ , with  $0 \leq \phi \leq 2\pi$ . Fig. 12.12.2 plots  $G_a$  versus the angle  $\phi$ . We note that the gain varies between the limits  $12.22 \leq G_a \leq 14.81$  dB.

 


Fig. 12.12.2 Variation of available gain around the noise figure circle  $F = 1.8$  dB.

The maximum value,  $G_a = 14.81$  dB, is reached when  $I_G = 0.4478 \angle -169.73^\circ$ , with a resulting matched load  $I_L = I_{out}^* = 0.5574 \angle 52.50^\circ$ . The two points  $I_G, I_L$ , as well as the

 


Fig. 12.12.3 Maximum available gain for given noise figure.

$G_a = 14.81$  dB gain circle, which is tangential to the 1.8-dB noise figure circle, are shown in Fig. 12.12.3.

The following MATLAB code performs these calculations and plots:

```
phi = linspace(0,2*pi,721);
gG = c2 + r2*exp(j*pi*phi);
G = db(Sgain(S,gG,'a'));
plot(phi*pi/180/pi, G);

[Ga, i] = max(G);

gammaG = gG(i);
gammaML = conj(gout(S,gammaG));

[ca, ra] = sgcirc(S, 'a', Ga);

smith; smithcir(c2, r2); smithcir(ca, ra);
plot([gammaG, gammaML], 'r');
```

The maximum gain and the point of tangency with the noise figure circle are determined by direct search, that is, evaluating the gain around the 1.8-dB noise figure circle and finding where it reaches a maximum.

The input and output stub matching networks can be designed with the help of the function stub1. The normalized source and load impedances are:

$$z_G = \frac{1 + I_G}{1 - I_G} = 0.3840 - 0.0767j, \quad z_L = \frac{1 + I_L}{1 - I_L} = 1.0904 + 1.3993j$$

The stub matching networks have lengths:

$$\text{stub1}(z_G^*, 'po') = \begin{bmatrix} 0.3749 & 0.3977 \\ 0.1251 & 0.0738 \end{bmatrix}, \quad \text{stub1}(z_L^*, 'po') = \begin{bmatrix} 0.3519 & 0.0991 \\ 0.1481 & 0.2250 \end{bmatrix}$$

The lower solutions have shorter total lengths  $d + l$ . The implementation of the matching networks with microstrip lines will be similar to that in Fig. 12.8.4. □

If the two-port is potentially unstable, one must be check that the resulting solutions for  $I_G, I_L$  both lie in their respective stability regions. Problems 12.6 and 12.7 illustrate the design of such potentially unstable low noise microwave amplifiers.

### 12.13 Problems

12.1 Using the relationships (12.4.3) and (12.4.6), derive the following identities:

$$(Z_{11} + Z_G)(Z_{22} + Z_L) - Z_{12}Z_{21} = \tag{12.13.1}$$

$$(Z_{22} + Z_L)(Z_{in} + Z_G) = (Z_{11} + Z_G)(Z_{out} + Z_L)$$

$$(1 - S_{11}I_G)(1 - S_{22}I_L) - S_{12}S_{21}I_GI_L = \tag{12.13.2}$$

$$(1 - S_{22}I_L)(1 - I_{in}I_G) = (1 - S_{11}I_G)(1 - I_{out}I_L)$$

Using Eqs. (12.4.4) and (12.4.5), show that:

$$\frac{Z_{21}}{Z_{22} + Z_L} = \frac{S_{21}}{1 - S_{22}I_L} \frac{1 - I_L}{1 - I_{in}}, \quad \frac{Z_{21}}{Z_{11} + Z_G} = \frac{S_{21}}{1 - S_{11}I_G} \frac{1 - I_G}{1 - I_{out}} \tag{12.13.3}$$

$$\frac{2Z_0}{Z_{in} + Z_G} = \frac{(1 - I_{in})(1 - I_G)}{1 - I_{in}I_G}, \quad \frac{2Z_0}{Z_{out} + Z_L} = \frac{(1 - I_{out})(1 - I_L)}{1 - I_{out}I_L} \tag{12.13.4}$$

Finally, for the real part  $R_L = \text{Re}(Z_L)$ , show that:

$$Z_L = Z_0 \frac{1 + I_L}{1 - I_L} \Rightarrow R_L = Z_0 \frac{1 - |I_L|^2}{|1 - I_L|^2} \tag{12.13.5}$$

12.2 *Computer Experiment.* The Hewlett-Packard ATF-10136 GaAs FET transistor has the following S-parameters at 4 GHz and 8 GHz [854]:

$$S_{11} = 0.54 \angle -120^\circ, \quad S_{21} = 3.60 \angle 61^\circ, \quad S_{12} = 0.137 \angle 31^\circ, \quad S_{22} = 0.22 \angle -49^\circ$$

$$S_{11} = 0.60 \angle 87^\circ, \quad S_{21} = 2.09 \angle -32^\circ, \quad S_{12} = 0.21 \angle -36^\circ, \quad S_{22} = 0.32 \angle -48^\circ$$

Determine the stability parameters, stability circles, and stability regions at the two frequencies.

12.3 Derive the following relationships, where  $R_G = \text{Re}(Z_G)$ :

$$\frac{Z_0 + Z_G}{2\sqrt{R_G Z_0}} = \frac{1}{\sqrt{|1 - I_G|^2}} \frac{|1 - I_G|}{1 - I_G}, \quad \frac{Z_0 - Z_G}{2\sqrt{R_G Z_0}} = -\frac{I_G}{\sqrt{|1 - I_G|^2}} \frac{|1 - I_G|}{1 - I_G}$$

12.4 Derive Eqs. (12.7.13) relating the generalized S-parameters of power waves to the conventional S-parameters.

12.5 Derive the expression Eq. (12.6.20) for the maximum available gain  $G_{MAG}$ , and show that it is the maximum of all three gains, that is, transducer, available, and operating gains.

12.6 *Computer Experiment.* The microwave transistor of Example 12.11.2 has the following noise parameters at a frequency of 1 GHz [854]:  $F_{\min} = 1.3$  dB,  $r_n = 0.16$ , and  $I_{Gopt} = 0.06 \angle 49^\circ$ .

Determine the matched load  $I_{Lopt}$  corresponding to  $I_{Gopt}$  and calculate the available gain. Then, plot the noise figure circles for  $F = 1.4, 1.5, 1.6$  dB.

For the 1.5-dB noise figure circle, determine the values of  $I_G, I_L$  that correspond to the maximum possible available gain.

Design microstrip stub matching circuits for the computed values of  $I_G, I_L$ .



12.7 *Computer Experiment.* The Hewlett-Packard ATF-36163 pseudomorphic high electron mobility transistor (PHEMT) has the following  $S$ - and noise parameters at 6 GHz [854]:

$$S_{11} = 0.75 \angle -131^\circ, \quad S_{21} = 3.95 \angle 55^\circ, \quad S_{12} = 0.13 \angle -12^\circ, \quad S_{22} = 0.27 \angle -116^\circ$$

$$F_{\min} = 0.66 \text{ dB}, \quad r_n = 0.15, \quad \Gamma_{G\text{opt}} = 0.55 \angle 88^\circ$$

Plot the  $F = 0.7, 0.8, 0.9$  dB noise figure circles. On the 0.7-dB circle, determine the source reflection coefficient  $\Gamma_G$  that corresponds to maximum available gain, and then determine the corresponding matched load coefficient  $\Gamma_L$ .

Design microstrip stub matching circuits for the computed values of  $\Gamma_G, \Gamma_L$ .